

CHAPTER: 5

Combinational

logic

Analysis

BASIC COMBINATIONAL LOGIC CIRCUITS :-

Example 5-1


In a certain chemical processing plant, a liquid chemical is used in a manufacturing process. The chemical is stored in three different tanks. A level sensor in each tank produces a HIGH voltage when the level of chemical in the tank drops below a specified point.

Design a circuit that monitors the chemical level in each tank and indicates when the level in any

two of the tanks drops below the specified point.

solution:

The AND-OR circuit in figure has inputs from sensors on tanks A, B and C. The AND gate G_1 checks the levels in tanks A and B, gate G_2 checks tanks A and C, and gate G_3 checks tanks B and C. When the chemical level in any two of the tanks gets ~~too~~ too low, one of the AND gates will have HIGH on both of its inputs, causing its output to be HIGH and be the final output X from the OR gate is HIGH. This HIGH input is then used to activate an indicator such as lamp or audible alarm,

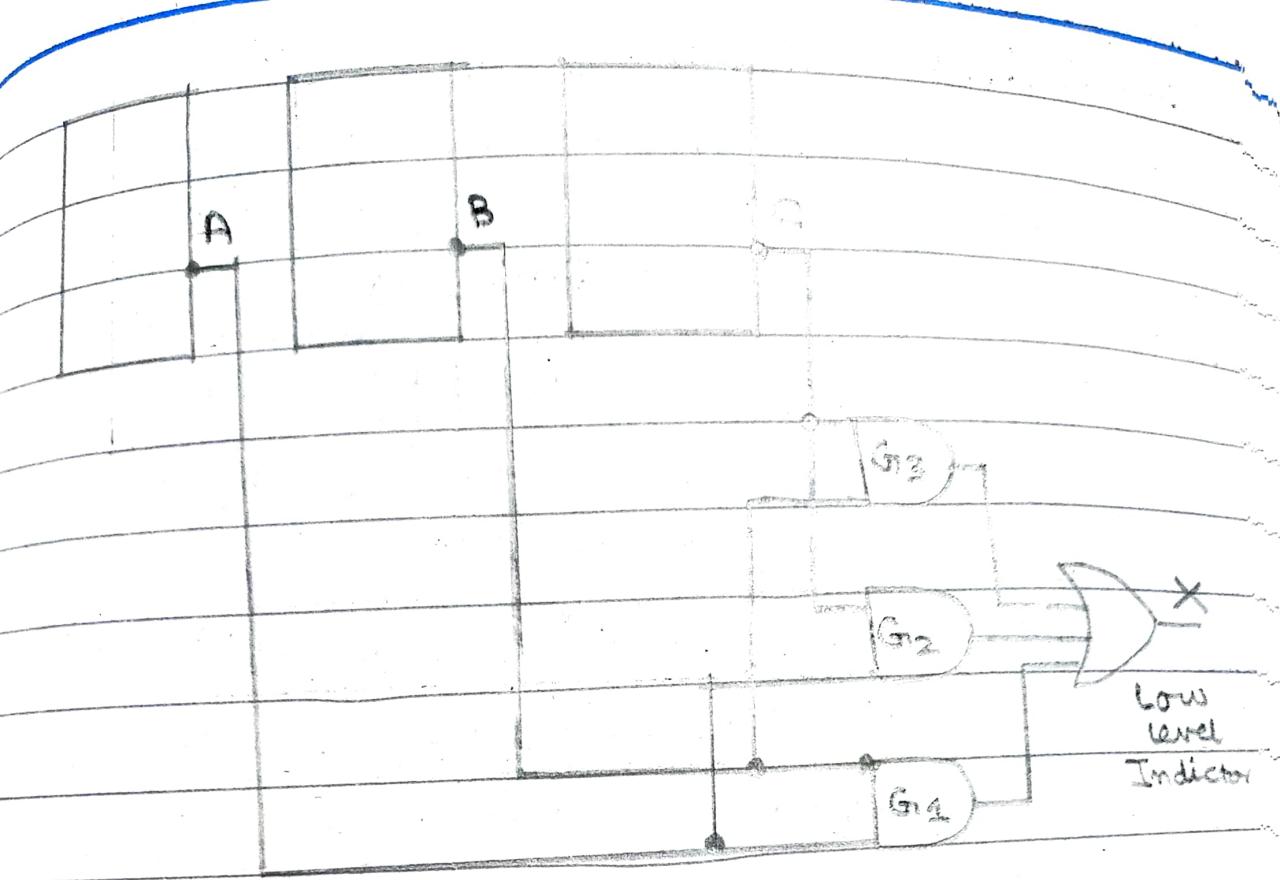


Example 5-2

The sensors in the chemical tanks of example 5-1 are being replaced by a new model! That produces a low voltage instead of a HIGH voltage when the level of the chemical in the tank drops below a critical point.

Modify the circuit to operate with the different input levels and still produce a HIGH output to activate the indicator when the level in any two of the tanks drops below the critical point. Show the logic diagram.

Solution:

The AND-OR invert circuit has inputs from the sensors on tanks A, B and C. The AND gate G_{11} checks the levels in tanks A and B, gate G_{12} checks tanks A and C and gate G_{13} checks tanks B and C. When the chemical level in any two of the tanks gets too low, each AND gate will have a LOW on at least one input, causing its output to be LOW and thus the final output X from the inverter is HIGH. This HIGH output is then used to activate an indicator.

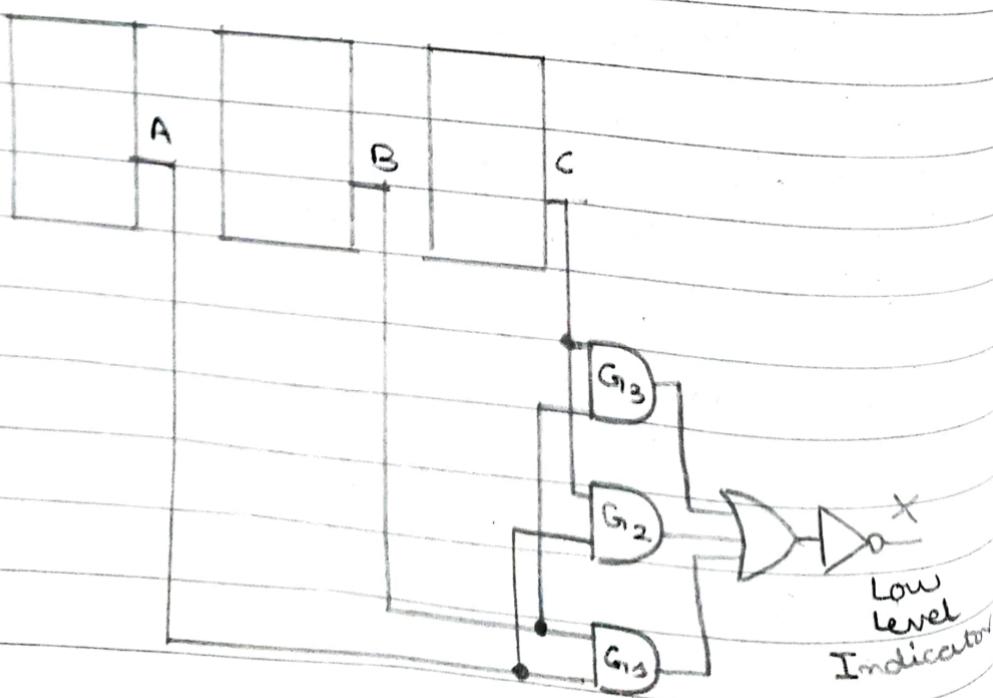


Example 5-3

Use exclusive-OR gates to implement an even-parity code generator for an original 4-bit code.

Solution:

A parity bit is added to a binary code in order to provide error detection. For even parity, a parity bit is added to the original code to make the total number of 1s in the code even.

The circuit in figure produces a 1 output when there is an odd number of 1s on the inputs in order to make the total number of 1s in the output code even. A 0 output is produced when there is an even number of 1s on the inputs.

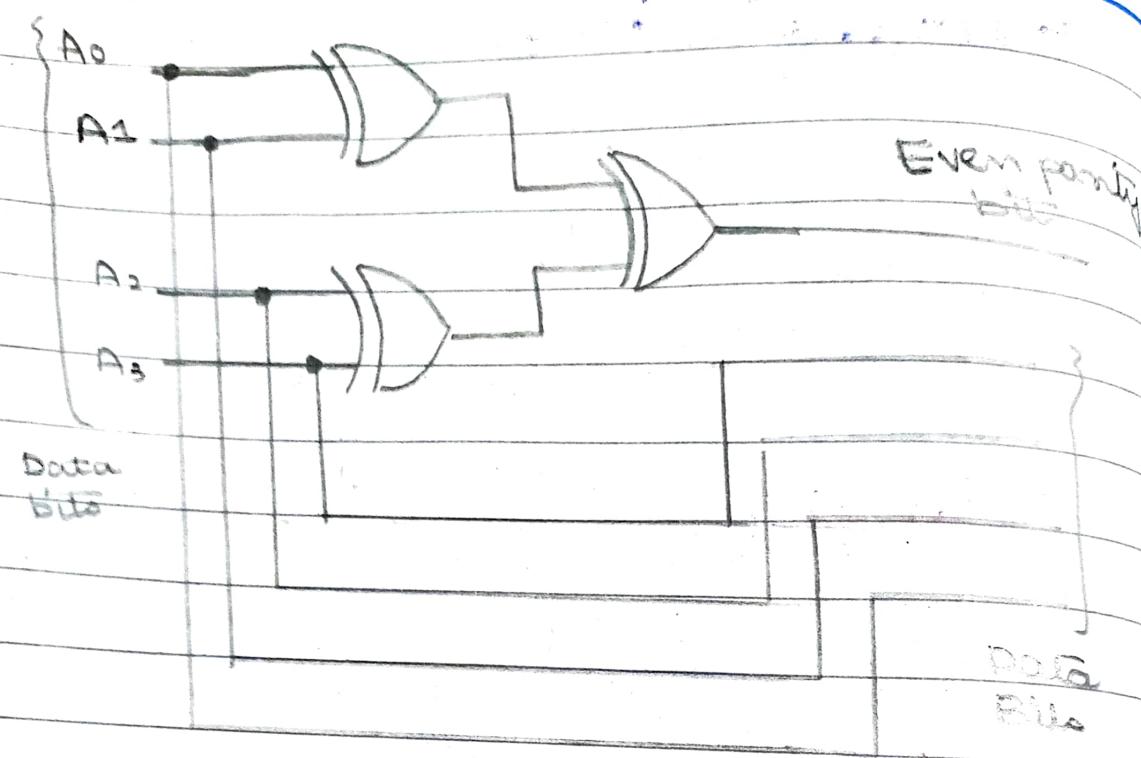


Example 5-4

Use exclusive-OR gates to implement an even parity checker for the 5-bit code generated by circuit in example 5-3.


Solution:

The circuit in figure produces a 1 output when there is an error in the five-bit code and a 0 when there is no error.

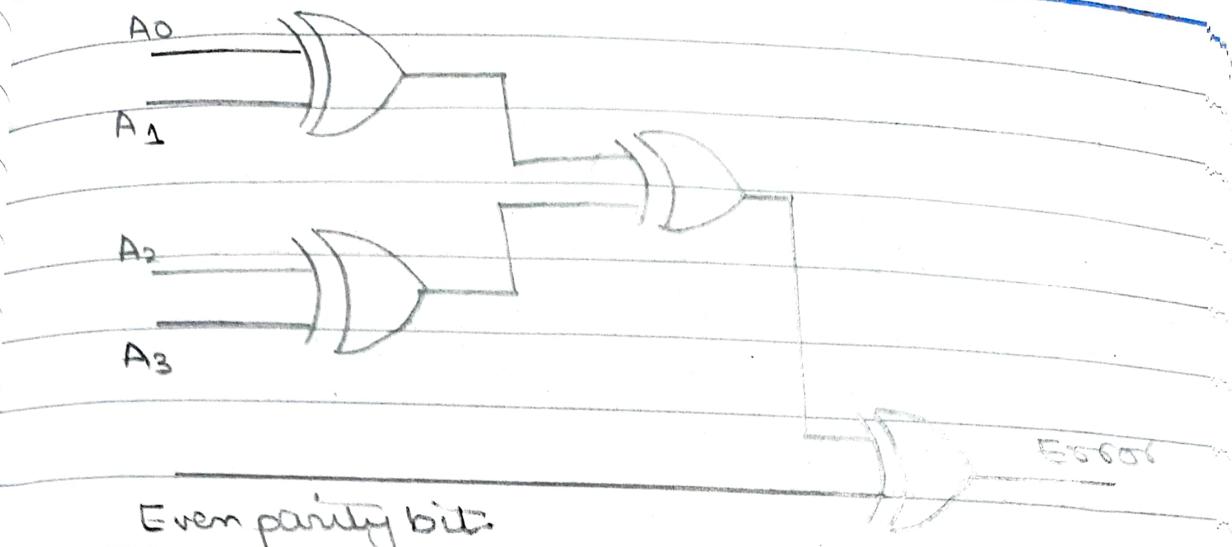


Section 5-1:

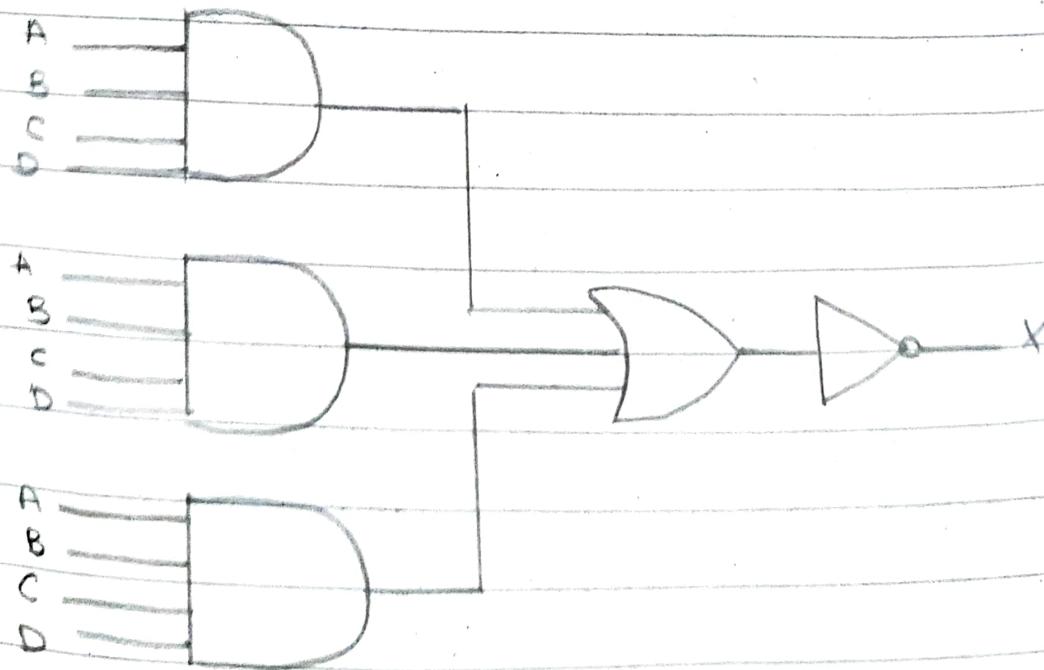
- 1.** Draw ANSI distinctive shape logic diagram for 4-wide, 3-input AND-OR-Invert circuit.
 Also draw the ANSI standard rectangular outline symbol.




Rectangular outline.

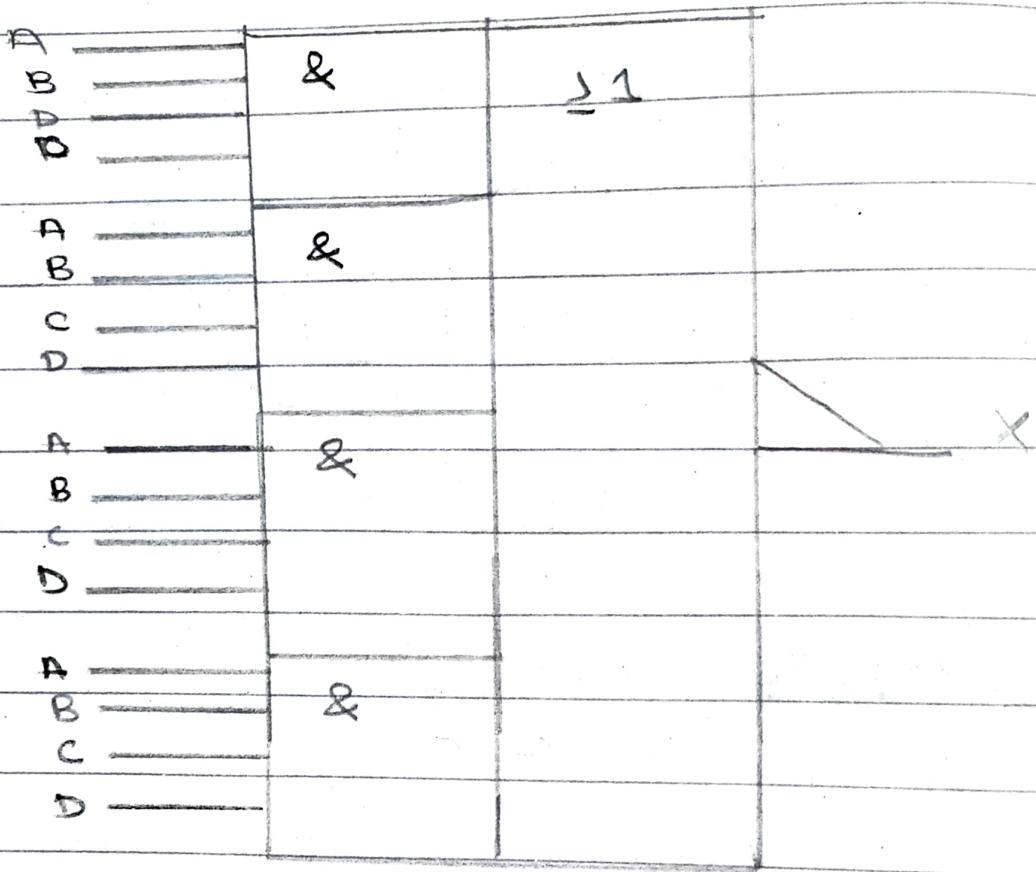

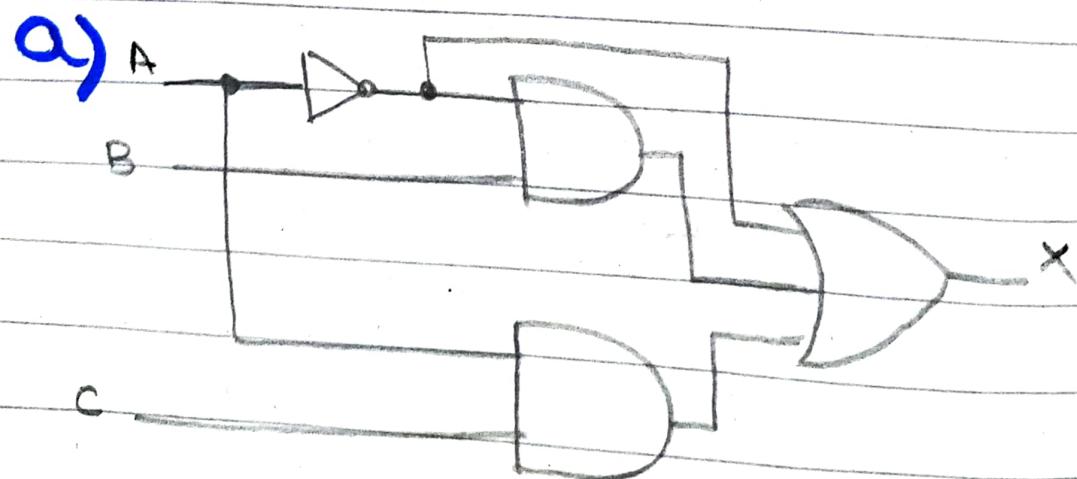2. Write output expression
for each circuit.



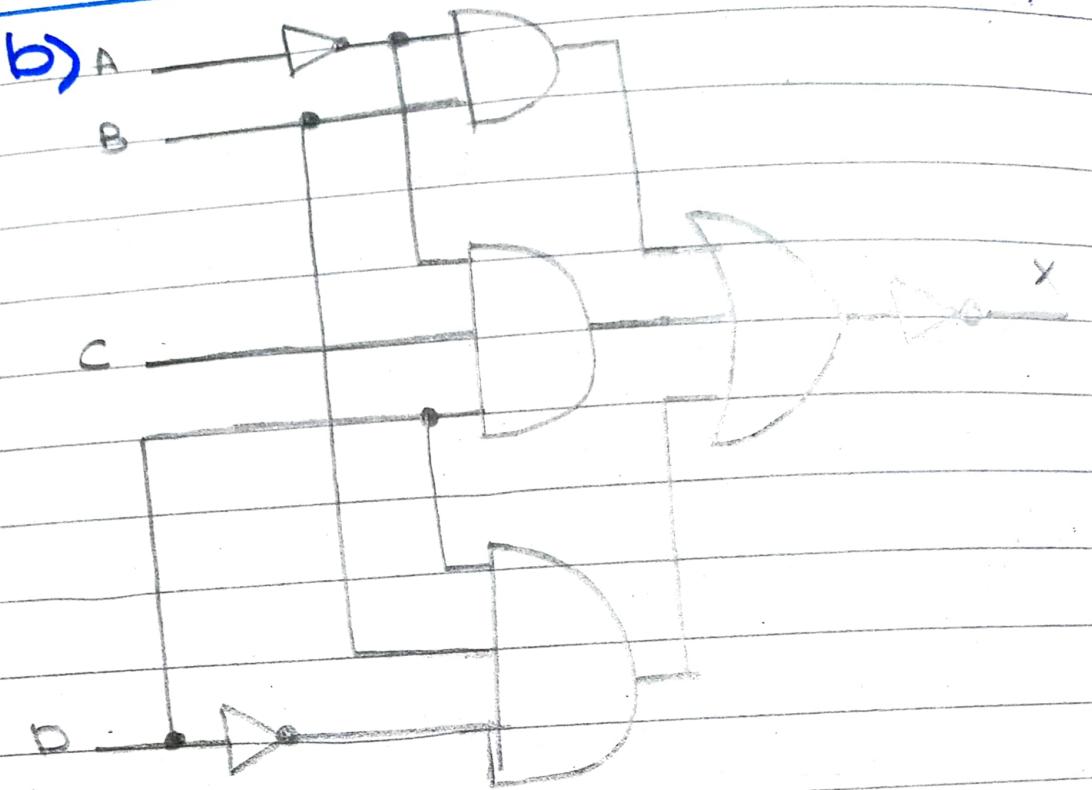
$$X = \overline{AB} + \overline{A} + AC$$




$$X = \overline{AB} + \overline{ACD} + DB\bar{D}$$

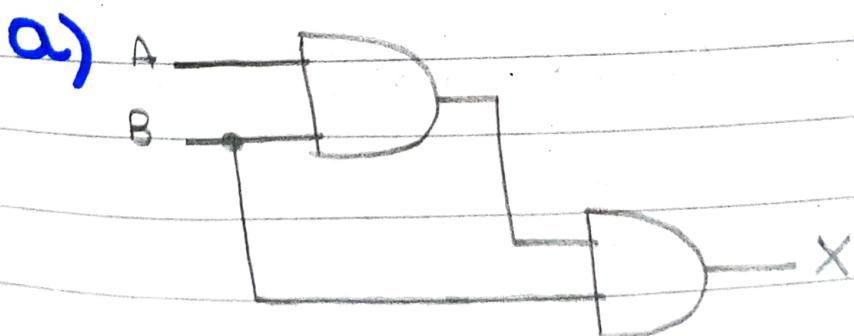3. Write output expression for each circuit as it appears.




$$X = ABB$$

b)

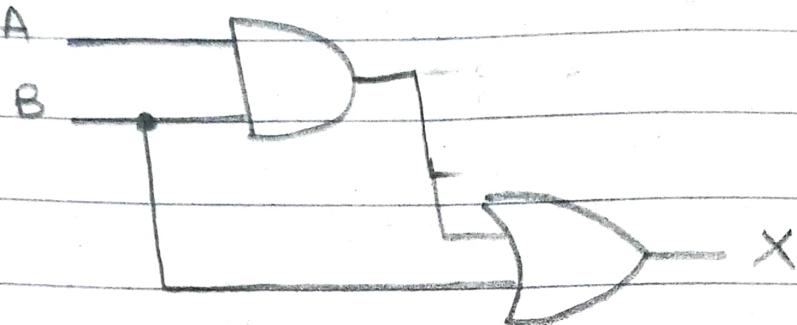


$$X = AB + B$$

c)

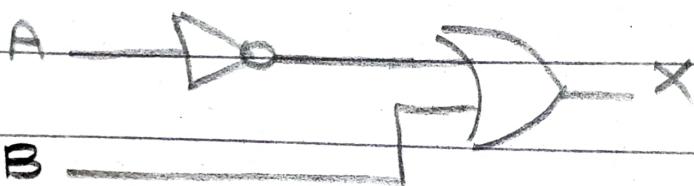


$$X = \overline{A} + B$$


d)

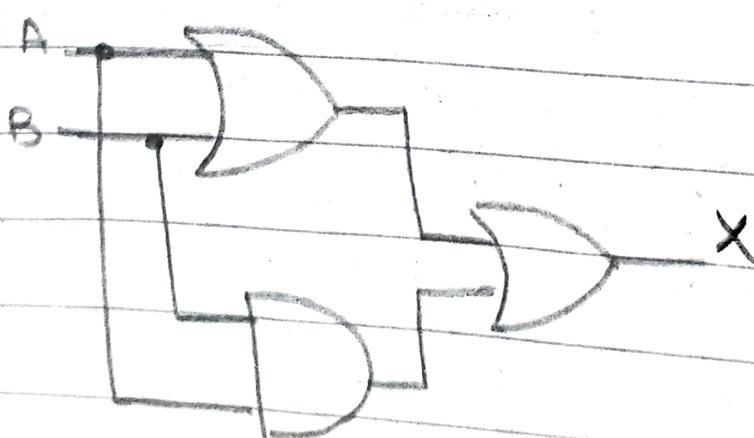

$$X = (A+B) + AB$$

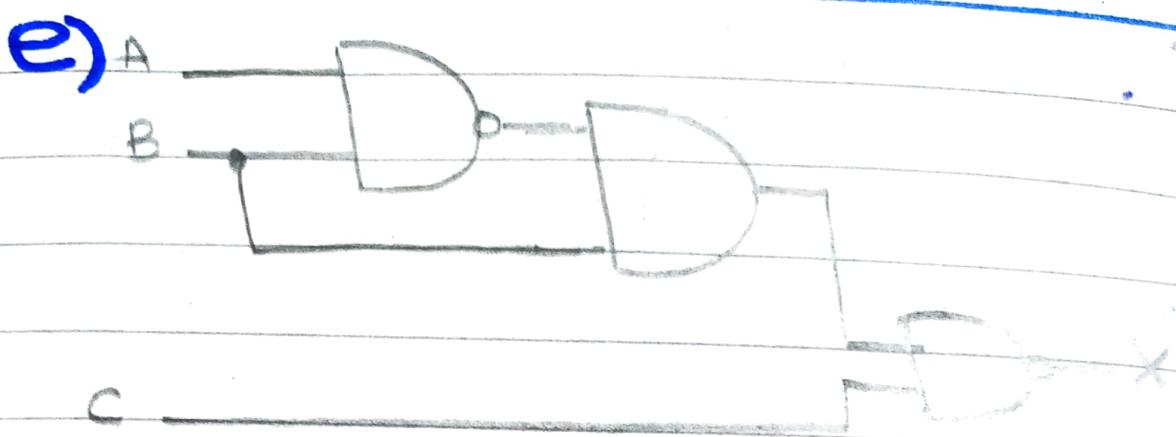

$$X = \overline{ABC}$$

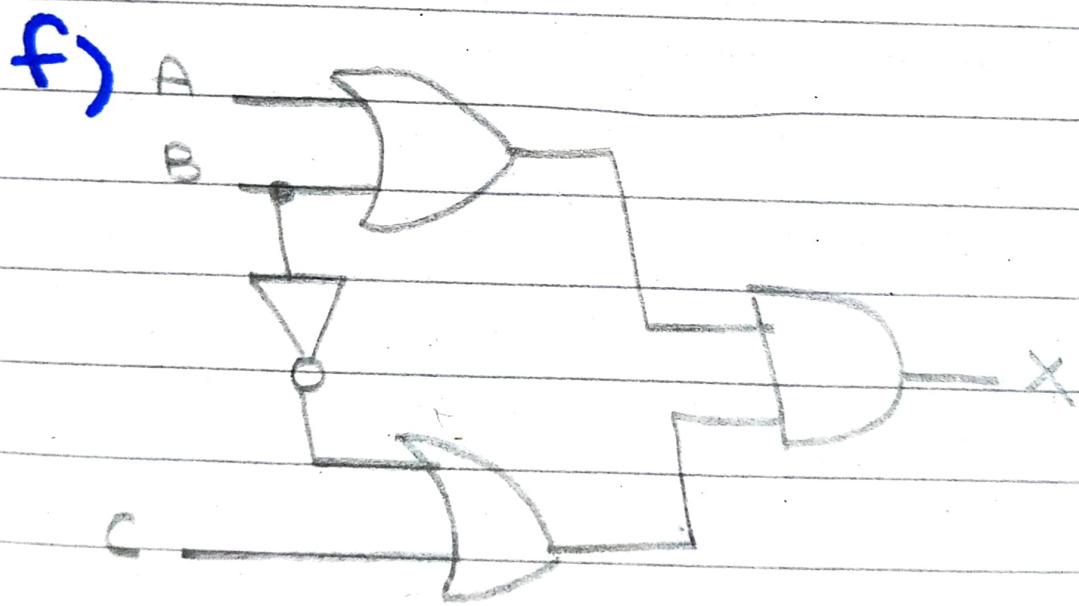

$$X = (A+B)(\overline{B}+C)$$

5. Develop truth table for each circuit in figure.

a) $X = ABB$

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1

b) $X = AB + B$

A	B	X
0	0	0
0	1	1
1	0	0
1	1	1

c) $X = \bar{A} + B$

A	B	X
0	0	1
0	1	1
1	0	0
1	1	1

d) $X = (A+B) + AB$

A	B	$A+B$	AB	X
0	0	0	0	0
0	1	1	0	1
1	0	1	0	1
1	1	1	1	1

e) $X = \overline{ABC}$

A	B	C	\overline{A}	X
0	0	0	1	1
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	0	1

f) $X = (A+B)(\bar{B}+C)$

A	B	C	\bar{B}	$A+B$	$\bar{B}+C$	X
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	0	0
0	1	1	0	1	1	1
1	0	0	1	1	1	1
1	0	1	1	1	1	1
1	1	0	0	1	0	0
1	1	1	0	1	1	1

IMPLEMENTING COMBINATIONAL LOGIC :-

Example 5-5

Design a logic circuit to implement the operation specified in truth table.


Inputs			X	Product Term
A	B	C		
0	0	0	0	
0	0	1	0	
0	1	0	0	
0	1	1	1	$\bar{A}BC$
1	0	0	0	
1	0	1	1	$\bar{A}\bar{B}C$
1	1	0	1	$A\bar{B}\bar{C}$
1	1	1	0	

solution:

Notice that $X=1$ for only three of the input conditions. Therefore, the logic expression is:

$$X = \bar{A}BC + A\bar{B}C + AB\bar{C}$$

The logic gates required are three invertors, 3-input AND gates and one 3-input OR gate.

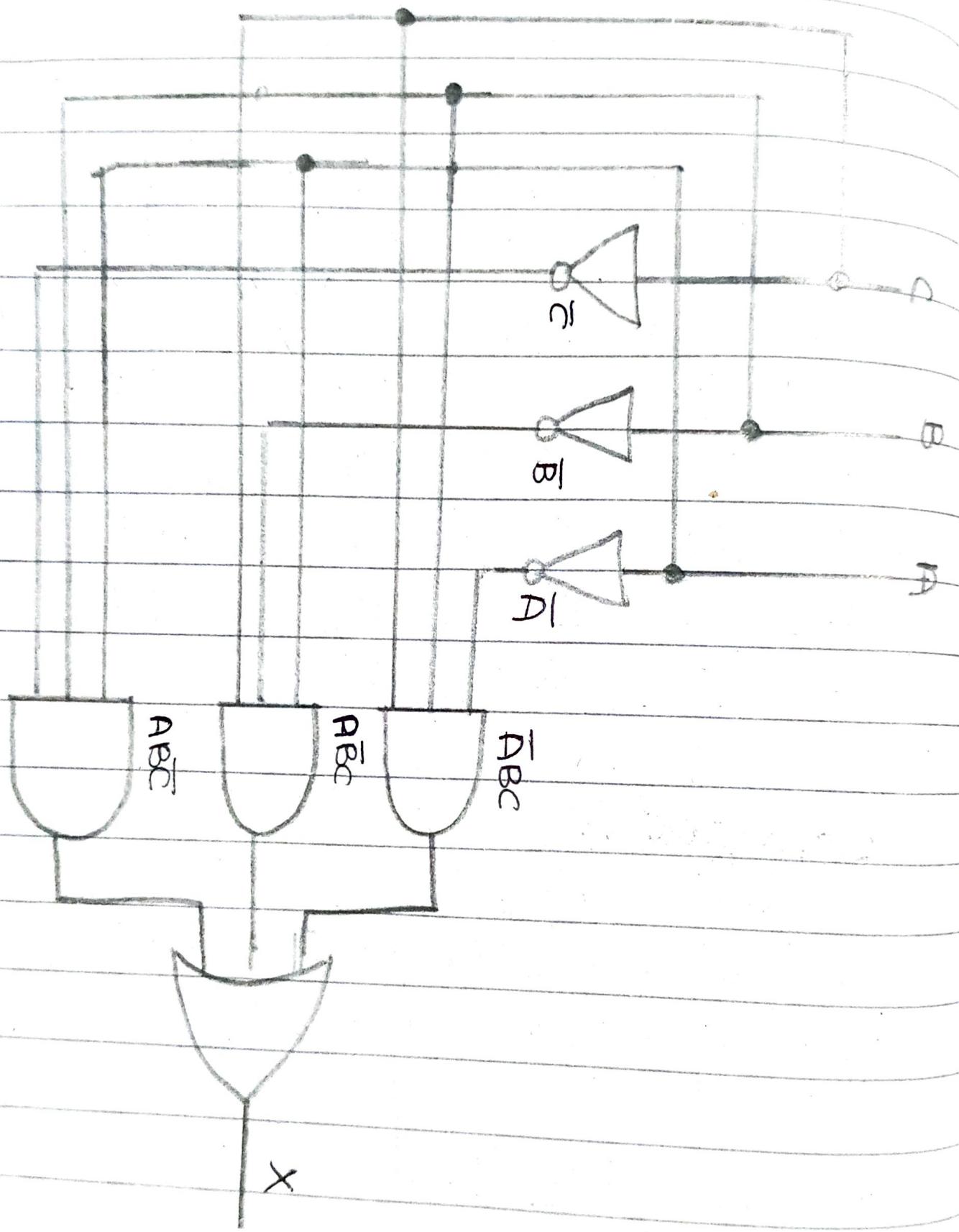

Example 5-6

Develop a logic circuit with four input variables, that will only produce a 1 output when exactly three input variables are 1.

Solution:


Out of sixteen possible combinations of four variables the combinations in which there are exactly three 1s are listed in table along with the corresponding product term for each.

A	B	C	D	Product Term
0	1	1	1	$\bar{A}BCD$
1	0	1	1	$A\bar{B}CD$
1	1	0	1	$AB\bar{C}D$
1	1	1	0	$ABC\bar{D}$

The product terms are OR-ed to get the following expression.


$$X = \bar{A}BCD + A\bar{B}CD + AB\bar{C}D + ABC\bar{D}$$

This expression is implemented in figure with AND-OR logic.

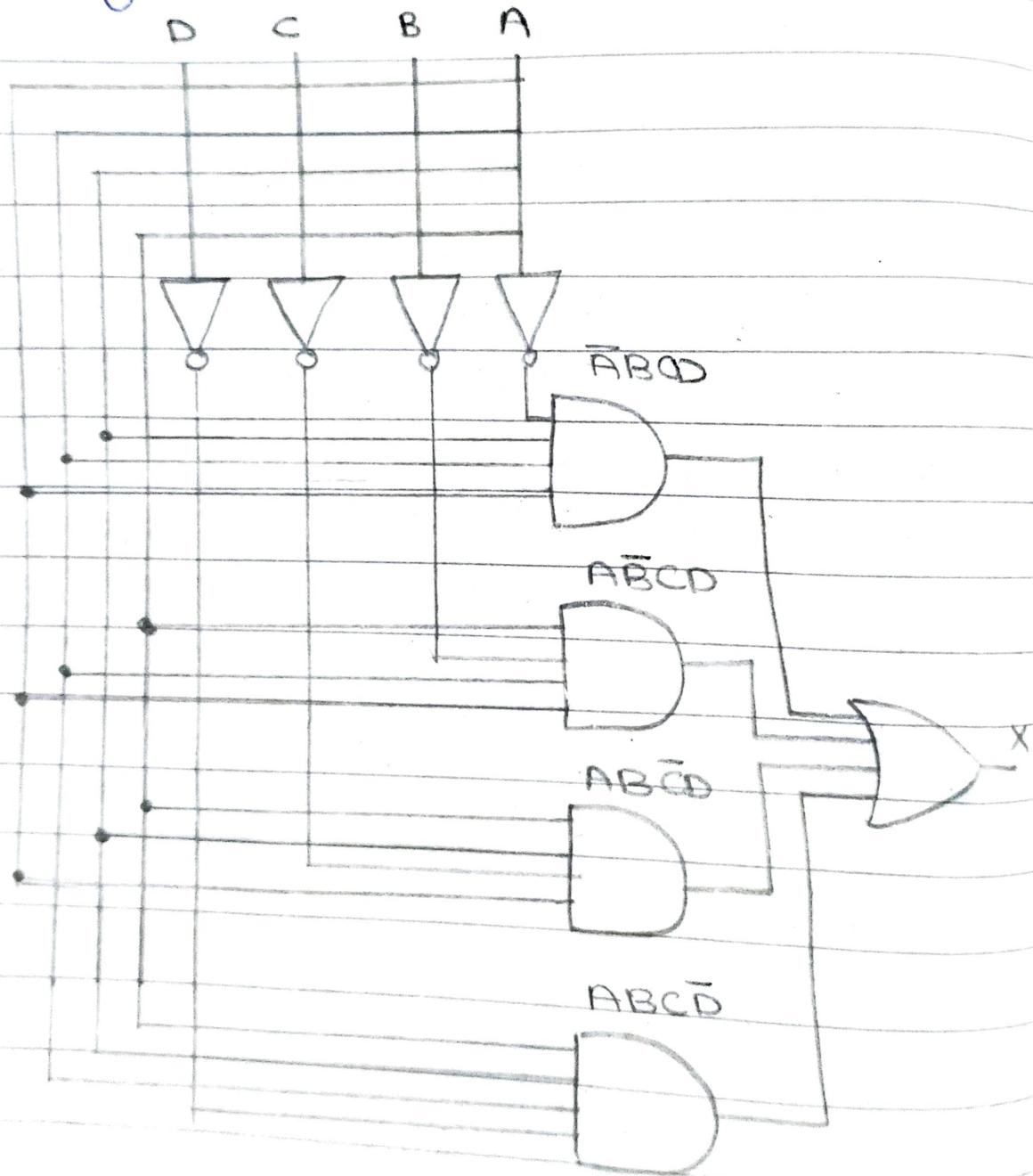

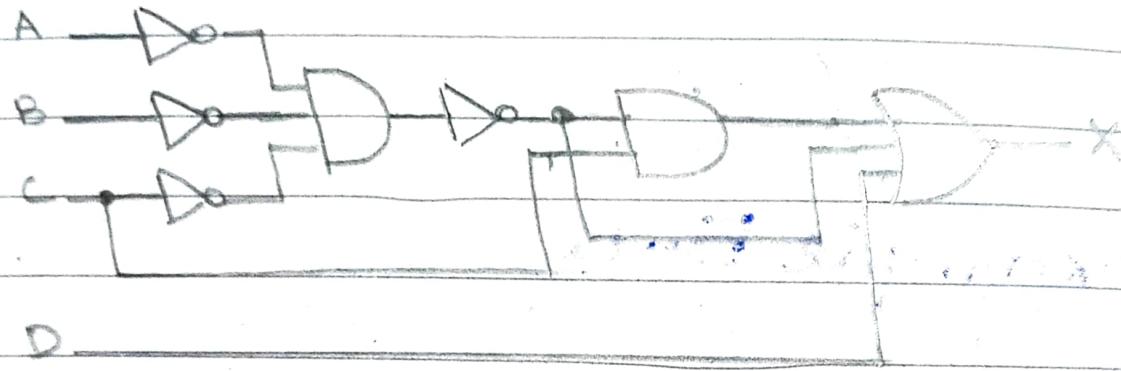Example 5-7

Reduce the combinational logic circuit in figure to a minimum form.



Solution:

The expression for output of the circuit is:


$$X = (\bar{A}\bar{B}\bar{C})C + \bar{A}\bar{B}\bar{C} + D$$

Applying DeMorgan's theorem and Boolean algebra,

$$\begin{aligned} X &= (\bar{A} + \bar{B} + \bar{C})C + \bar{A} + \bar{B} + \bar{C} + D \\ &= AC + BC + CC + A + B + C + D \\ &= AC + BC + C + A + B + \cancel{C} + D \\ &= C(A + B + 1) + A + B + D \end{aligned}$$


$$X = A + B + C + D$$

The simplified circuit is a 4-input OR gate.

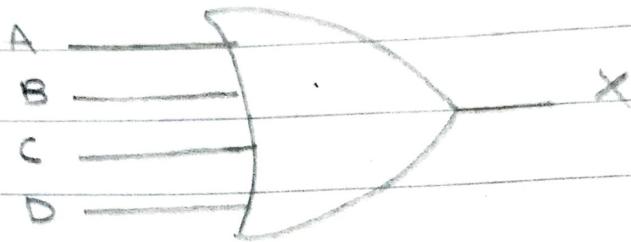

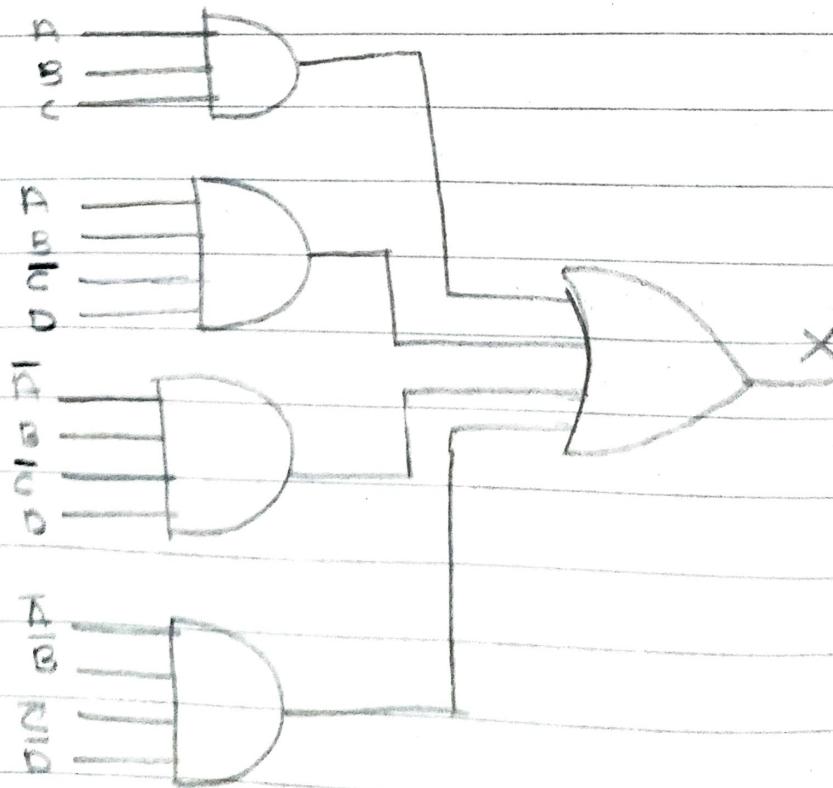Example 5-8

minimize the combinational logic circuit in figure. Inverters for the complement variables are not shown.



Solution :

The output expression is

$$X = \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D}$$


Expanding the first term to include the missing variables

D and \bar{D} .

$$\begin{aligned} X &= \bar{A}\bar{B}\bar{C} (D + \bar{D}) + A\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \\ &\quad \bar{A}\bar{B}C\bar{D} \\ &= \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}\bar{D} + \\ &\quad \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} \end{aligned}$$

This expanded SOP expression is mapped and simplified on the Karnaugh map in figure. The simplified implementation is shown. Inverters are not shown.

A	B	CD	00	01	11	10
00			1	1		
01						
11			1			
10			1	1		

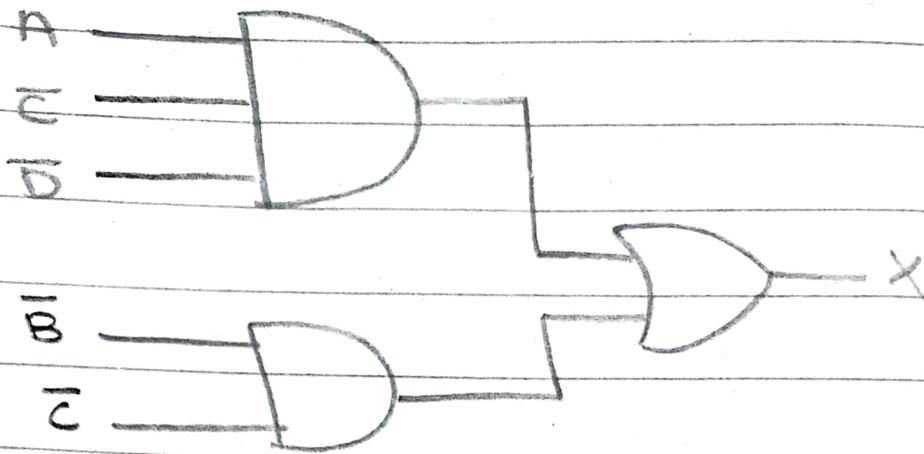


Section 5-2

8. Develop an AND-OR-Invert logic circuit for a power drive which switches on (logic 1) when the guard is in place (logic 1) and switches off (logic 0) when the motor is too hot (logic 0)

Let $G = \text{guard}$, $S = \text{switch}$,
 $M = \text{Motor temperature}$,
 $P = \text{Power}$.

$$\Rightarrow P = \overline{G}S + MS$$

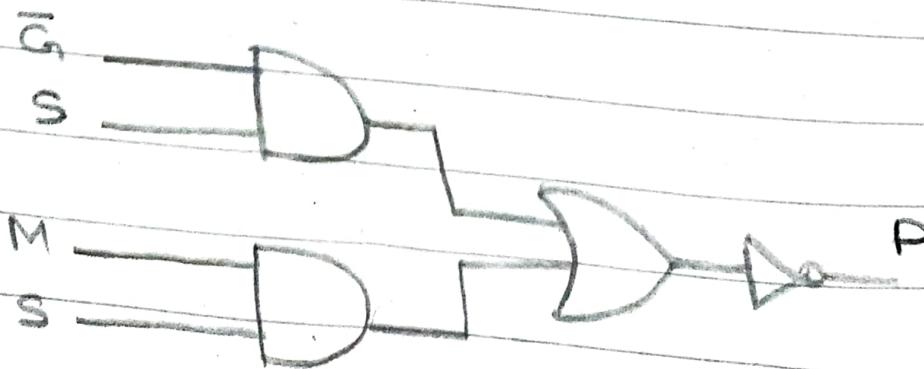


9. An AOI (AND - OR Invert) logic chip has two 4-input AND gates connected to a 2-input NOR gate. Write the Boolean expression for the circuit.

$$X = \overline{ABCD} + \overline{EFGH}$$

10. Use AND gates, OR gates or combinations of both to implement the following expressions as stated:


a) $X = A + B + C$

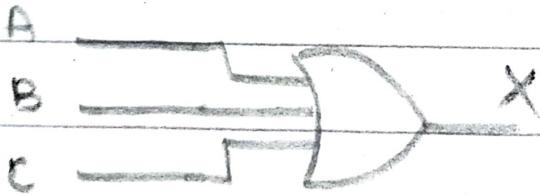


b) $X = ABC$




c) $X = A + BC$

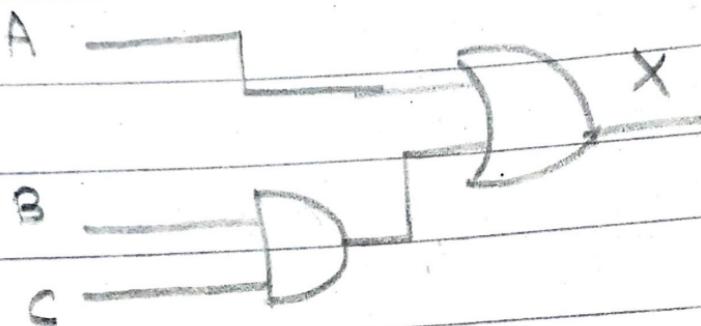


d) $X = AB + CD$

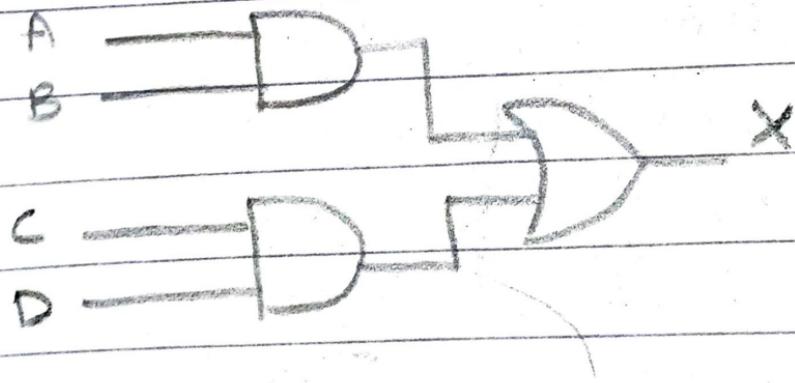


e) $X = (A+B)(C+D)$

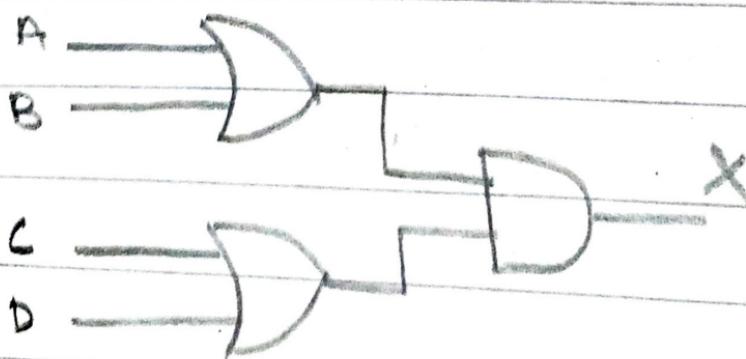

f) $X = A + BCD$

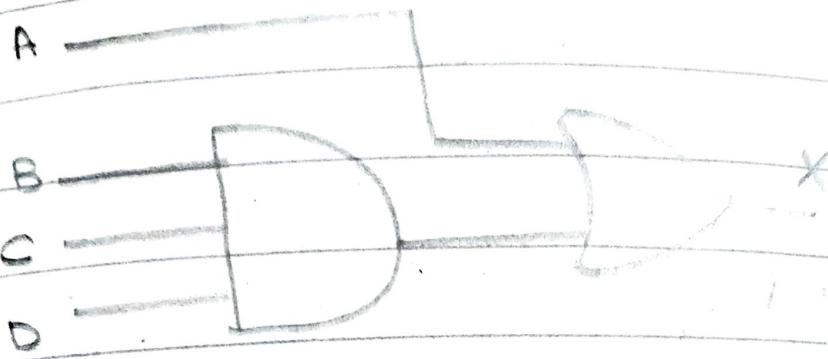


g) $X = ABC + BCD + DEF$

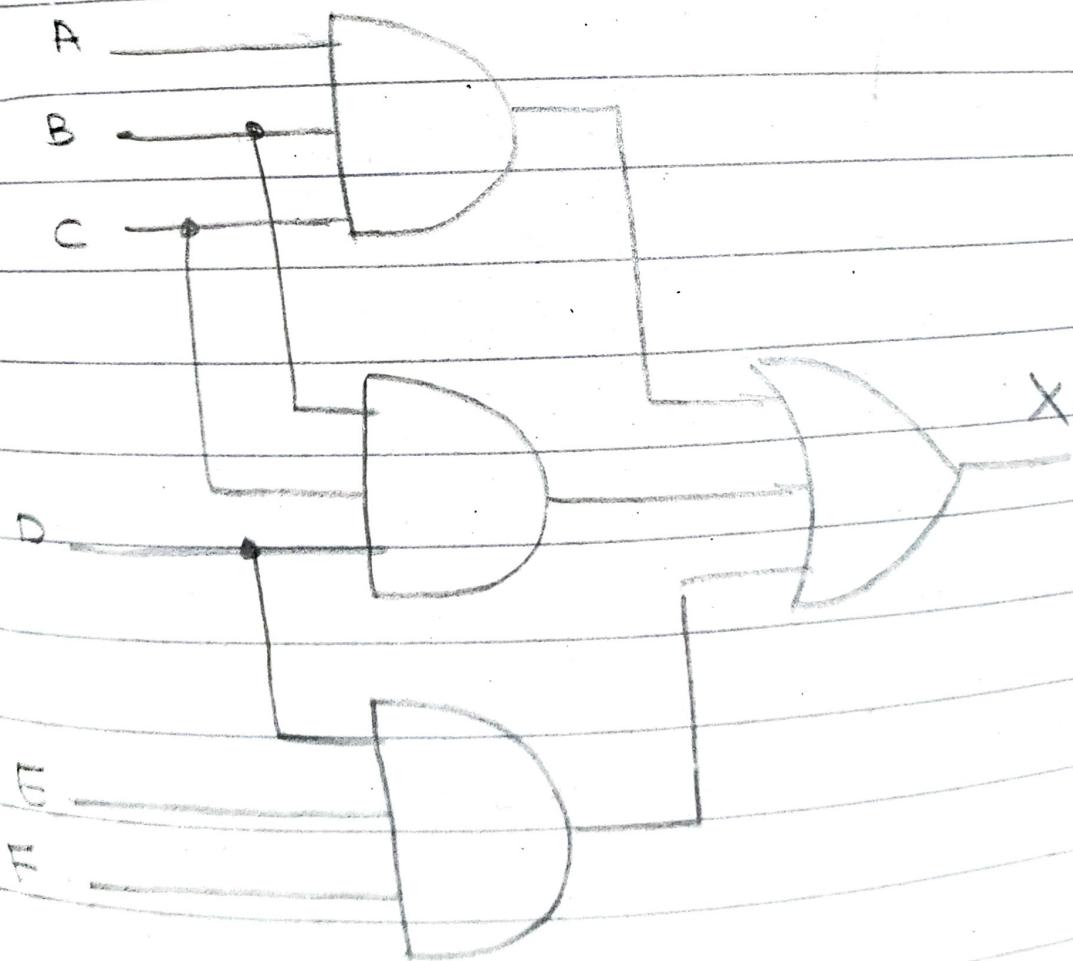


11. Use AND gates, OR gates and invertors as needed to implement the following logic expressions as stated:


a) $X = AB + \overline{BC}$

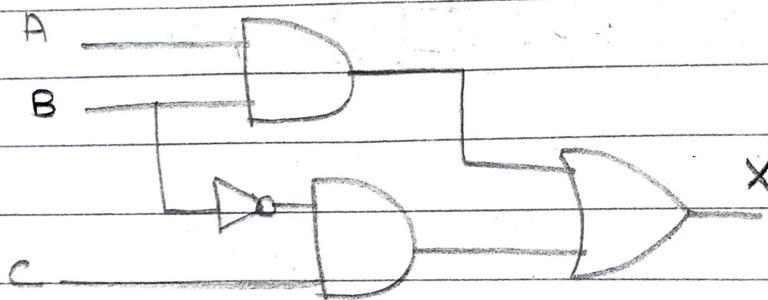


b) $X = A(B + \overline{C})$

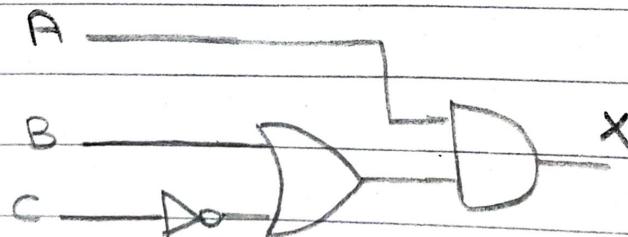

c) $X = A\overline{B} + AB$

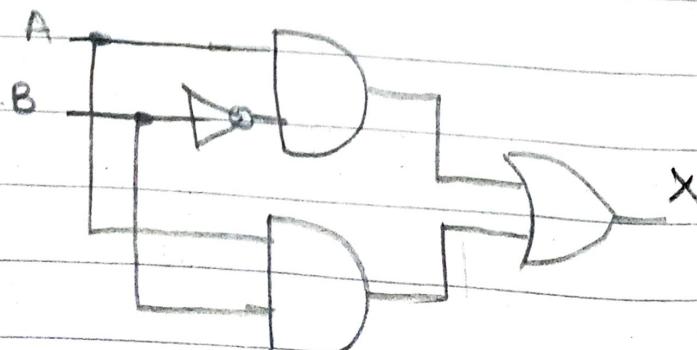

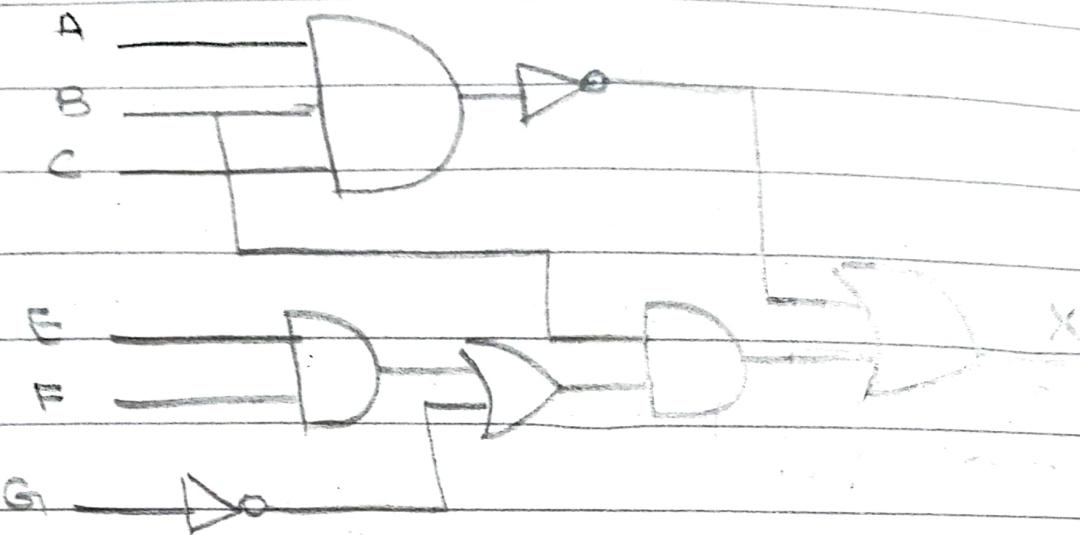d) $X = \overline{ABC} + B(EF + \overline{G})$



13. Implement a logic circuit
for the truth table.

Inputs			Output
A	B	C	X
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1


$$X = \overline{ABC} + \overline{A}B\overline{C} + A\overline{B}\overline{C} + \dots$$

$$ABC + A\overline{B}C$$


A	B	C	O	1
00			(1)	
01			(1)	
11			(1)	(1) → AB
10			(1)	

$\downarrow \overline{C}$

$X = AB + \overline{C}$

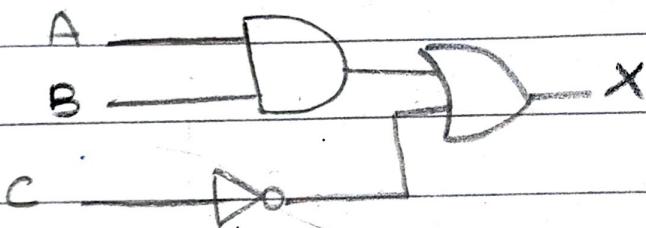

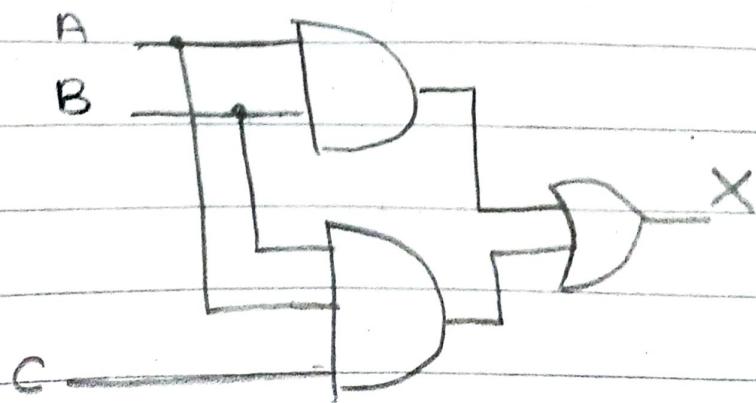15. Simplify the circuit as much as possible and verify that the simplified circuit is equivalent to the original by showing that the truth tables are identical.



$$\begin{aligned}
 X &= AB + ABC \\
 &= AB(1+C) \\
 &= AB
 \end{aligned}$$

A	B	C	AB	ABC	X
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	0	0
1	1	0	1	0	1
1	1	1	1	1	1

The value of X does not change what value of C is. It is depend on AB .

A	B	X
0	0	0
0	1	0
1	0	0
1	1	1



17. Minimize the gates required to implement the function in each part of Problem 11 in SOP form.

a) $X = AB + \bar{B}C$

A	B	C	O	1
0	0			(1)
0	1			
1	1		(1)	(1)
1	0			(1)

$$\begin{aligned}
 X &= AB(C + \bar{C}) + \bar{B}C(A + \bar{A}) \\
 &= ABC + ABC + A\bar{B}C + \bar{A}\bar{B}C
 \end{aligned}$$

No simplification possible.

b) $X = A(B + \bar{C})$

$$\begin{aligned}\Rightarrow X &= A(B + \bar{C}) \\ &= AB + A\bar{C} \\ &= AB(C + \bar{C}) + A\bar{C}(B + \bar{B}) \\ &= ABC + AB\bar{C} + A\bar{B}\bar{C} + A\bar{B}C \\ \Rightarrow X &= ABC + A\bar{B}C\end{aligned}$$

A	B	C	0	1
0	0	0		
0	1	0		
1	1	0	1	1
1	0	0		

$$X = AC$$

c) $X = AB + A\bar{B}$


$$\begin{aligned}\Rightarrow X &= AB + A\bar{B} \\ &= A(B + \bar{B}) \\ &= A(1) \\ &= A\end{aligned}$$

No simplifications.

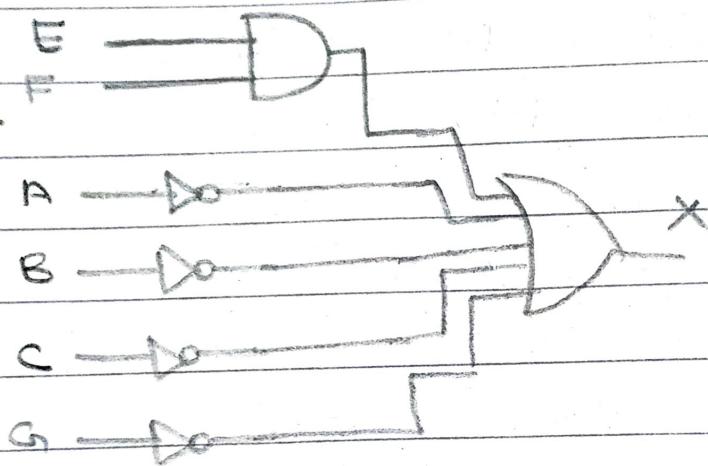d) $X = \overline{ABC} + B(EF + \overline{G})$

$$\Rightarrow X = \overline{A} + \overline{B} + \overline{C} + BEF + B\overline{G}$$

$$= \overline{A} + \overline{B} + \overline{C} + EF + \overline{G}$$



e) $X = A(BC(A+B+C+D))$

$$\Rightarrow X = A(BC(A+B+C+D))$$

$$= A(ABC + BBC + BCC + BCD)$$

$$= AABC + ABC + ABC + ABCD$$

$$= ABC + \cancel{ABC} + \cancel{ABC} + ABCD$$

$$= ABC + ABCD$$

$$= ABC(1 + D)$$

$$= ABC$$



18. Minimize the gates required to implement the functions in each part of Problem 12 in SOP form.

a) $X = \bar{A}B + CD + (\bar{A} + B)(ACD + \bar{B}E)$

$$\begin{aligned} \Rightarrow X &= \bar{A}B + CD + \bar{A}\bar{B}(ACD + \bar{B} + \bar{E}) \\ &= \bar{A}B + CD + \bar{A}\bar{B}ACD + \bar{A}\bar{B}\bar{B} + \end{aligned}$$

$$\bar{A}\bar{B}E$$


$$= \bar{A}B + CD + 0 + \bar{A}\bar{B} + \bar{A}\bar{B}E$$

$$= \bar{A}(B + \bar{B}) + CD + \bar{A}\bar{B}E$$

$$= \bar{A} + CD + \bar{A}\bar{B}E$$

$$= \bar{A}(1 + \bar{B}E) + CD$$


$$\Rightarrow X = \bar{A} + CD$$

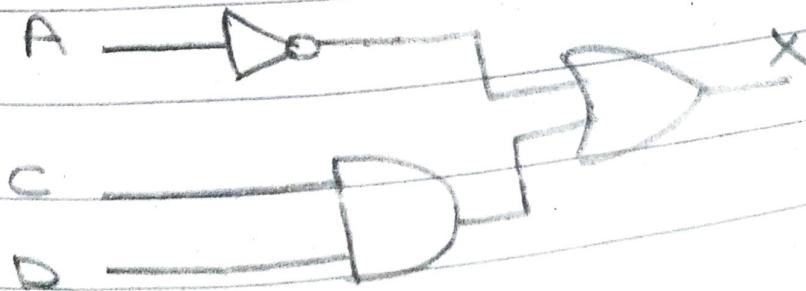

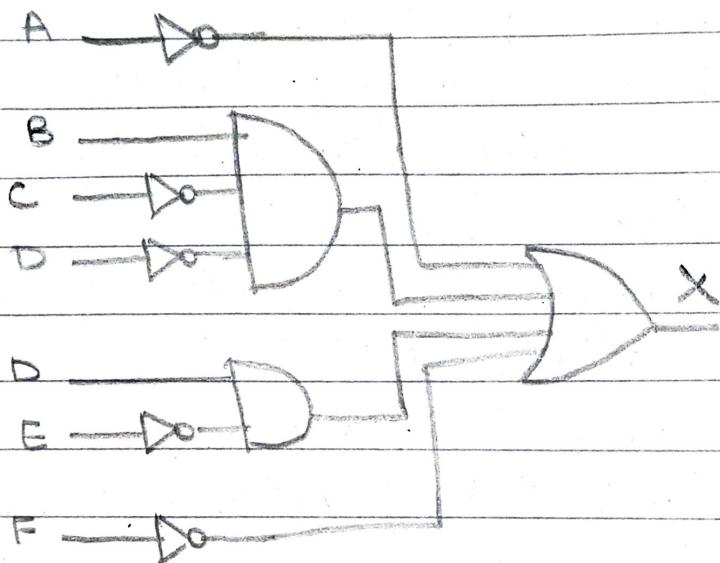b) $X = AB\overline{CD} + D\overline{EF} + \overline{AF}$

$$\Rightarrow X = ABC\overline{D} + DEF + \overline{A} + F$$

$$\Rightarrow X = B\overline{C}\overline{D} + DE + \overline{A} + F$$



c) $X = \overline{A}(B + \overline{C}(D+E))$

$$\Rightarrow X = \overline{A}(B + \overline{C}D + \overline{C}E)$$

$$\Rightarrow X = \overline{A}B + \overline{A}\overline{C}D + \overline{A}\overline{C}E$$

