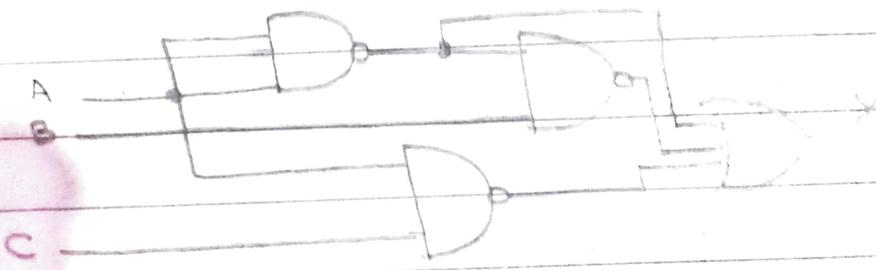


THE UNIVERSAL PROPERTY OF NAND AND NOR GATES:-


Section 5-3

20. Implement the logic circuits
using only NAND gates.

a)




b)

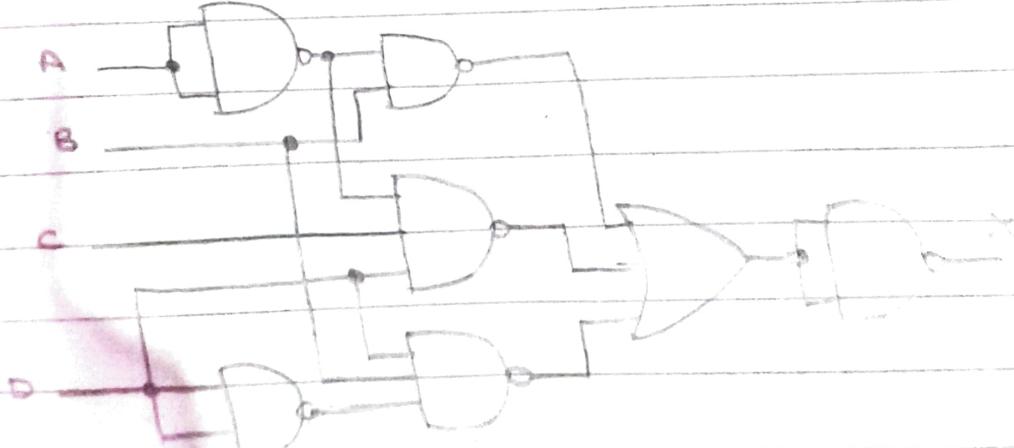


22. Repeat Problem 20 using
only NOR gate.

a)

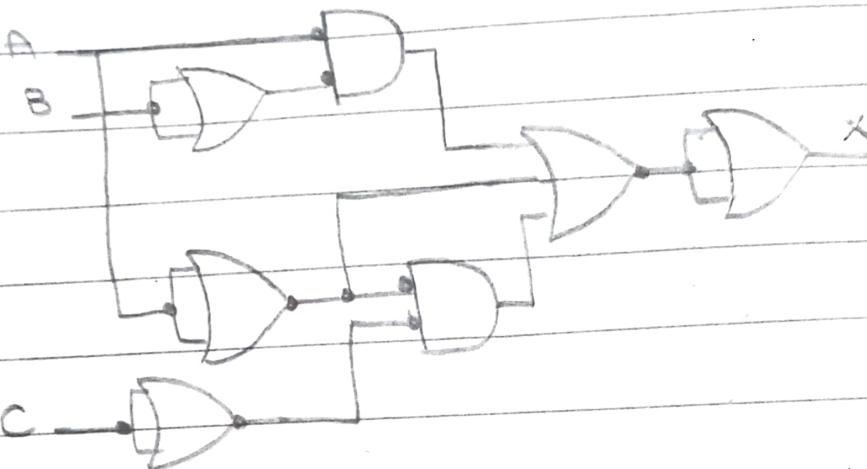


b)

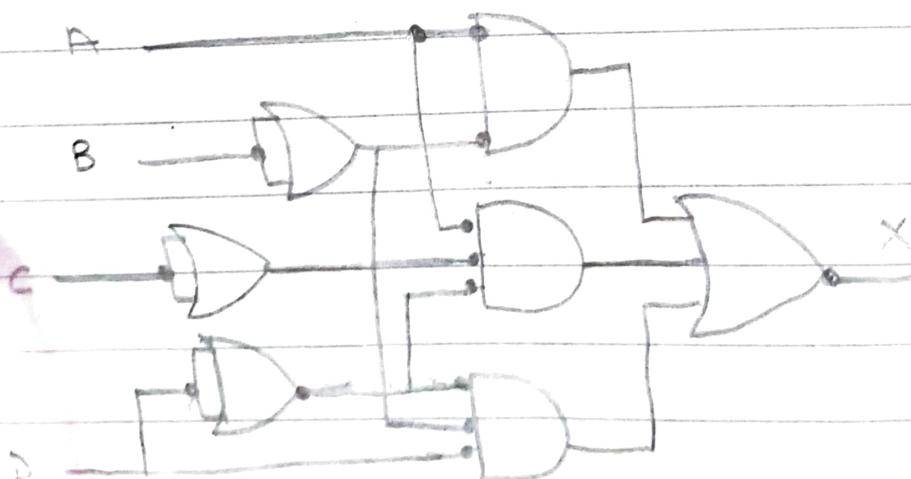

COMBINATIONAL LOGIC USING NAND AND NOR GATES:-

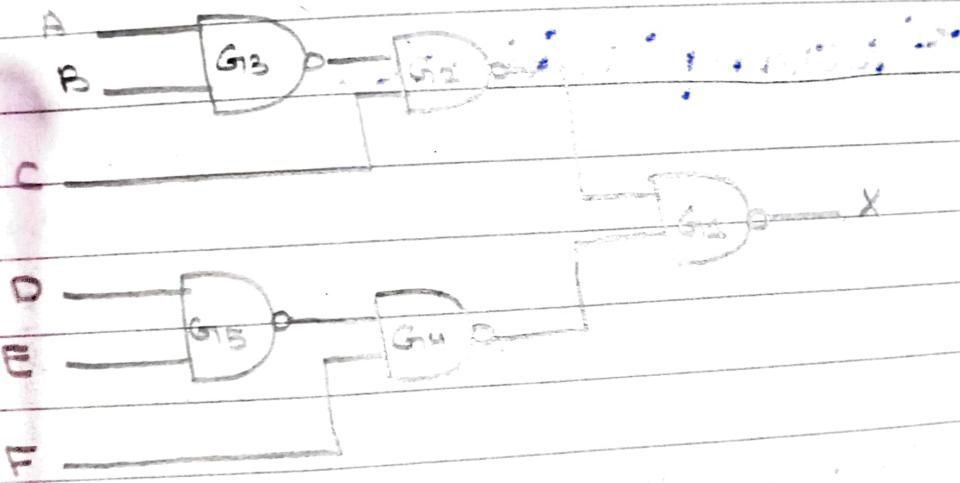Example 5-9


Redraw the logic diagram and develop the output expression for the circuit.



Solution:

Redraw the logic diagram with the use of equivalent negative-OR symbols. Writing the expression for X directly from the indicated logic operation from each gate gives

$$X = (\bar{A} + \bar{B})C + (\bar{D} + \bar{E})F$$

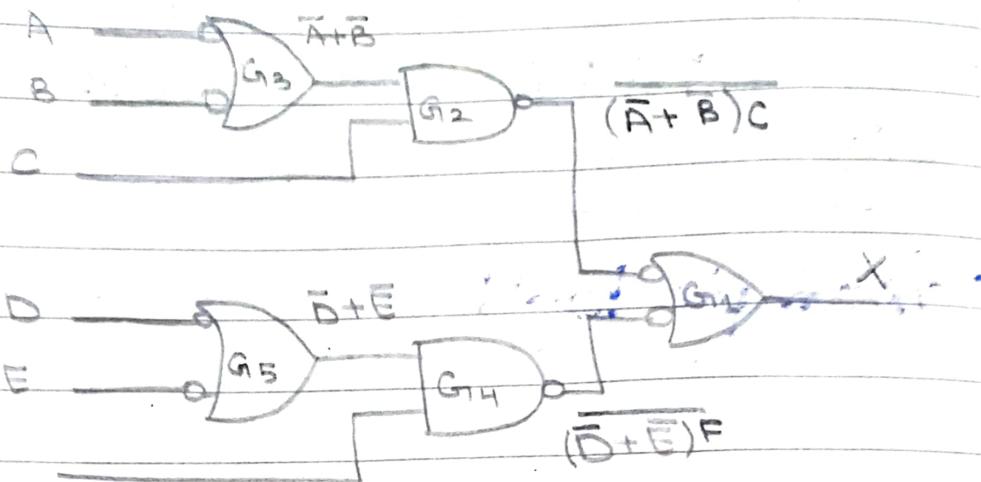


Example 5-10

Implement each expression with NAND logic using appropriate dual symbols.


a) $ABC + DE$

Solution:

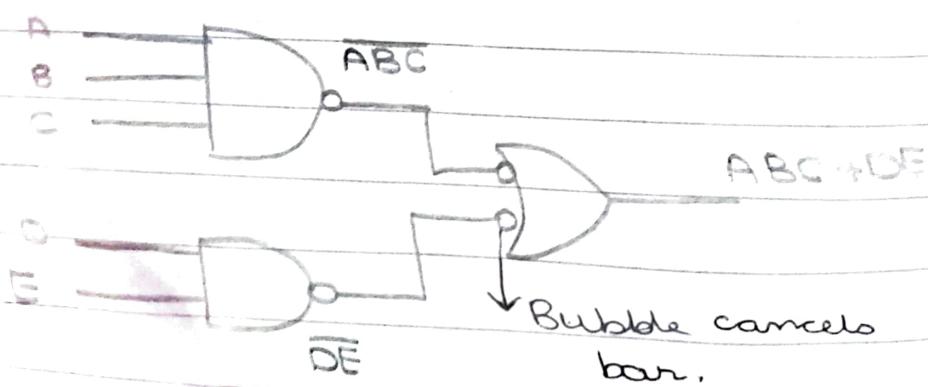

b) $ABC + \bar{D} + \bar{E}$

solution:

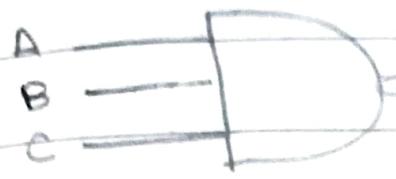

ABC

Bubble cancels
bars



D


ABC + D + E

E

Bubbles adds bars to
D and E

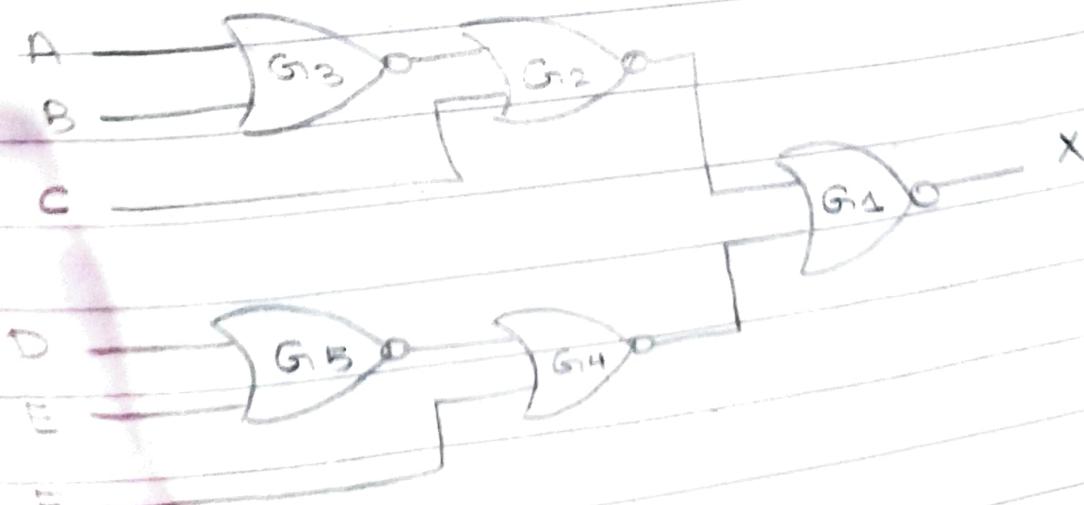Example 5-11


Using appropriate dual symbols,
redraw the logic diagram and
develop the output expression for
the circuit.



solution.

Redraw the logic diagram with the equivalent negative-AND symbols. Writing the expression for X directly from the indicated operation of each gate.


$$X = (\bar{A}\bar{B} + C)(\bar{D}\bar{E} + F)$$

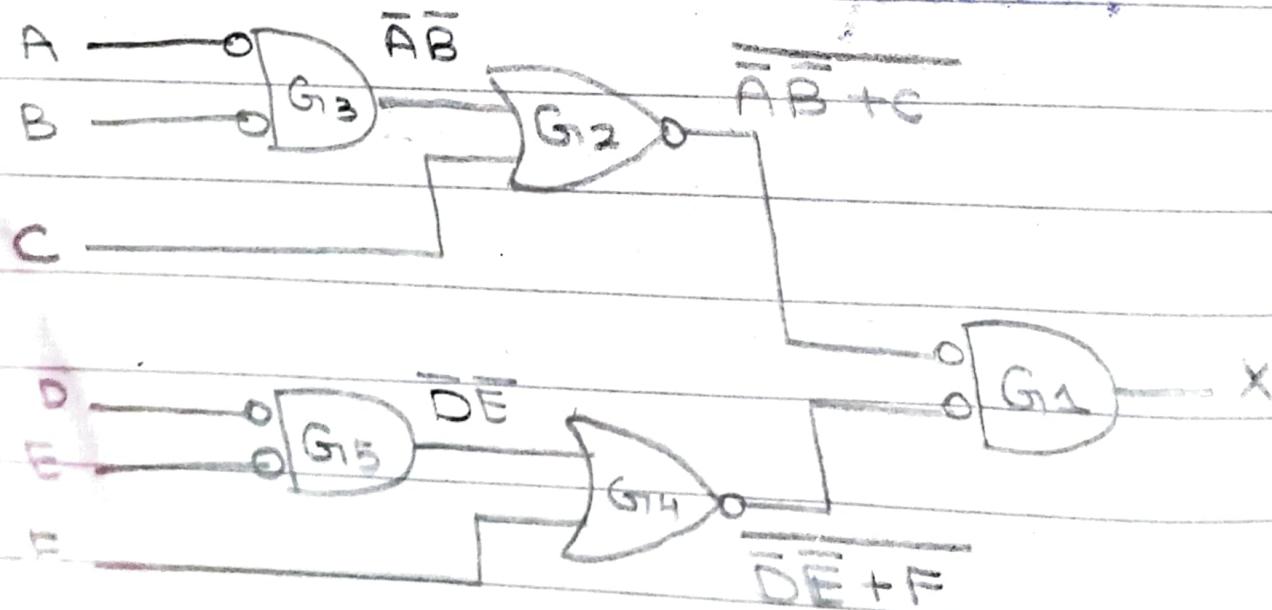


Section 5-4

24. Show how the following expressions can be implemented as stated using only NOR gates.


a) $X = ABC$

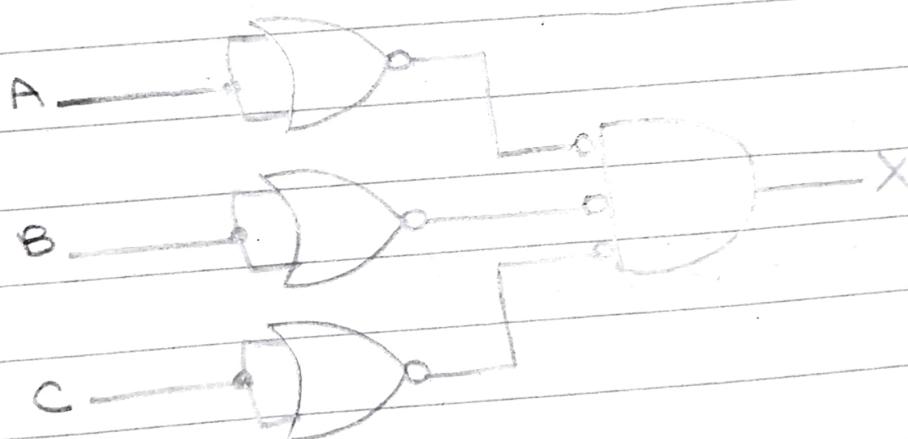


b) $X = \overline{ABC}$

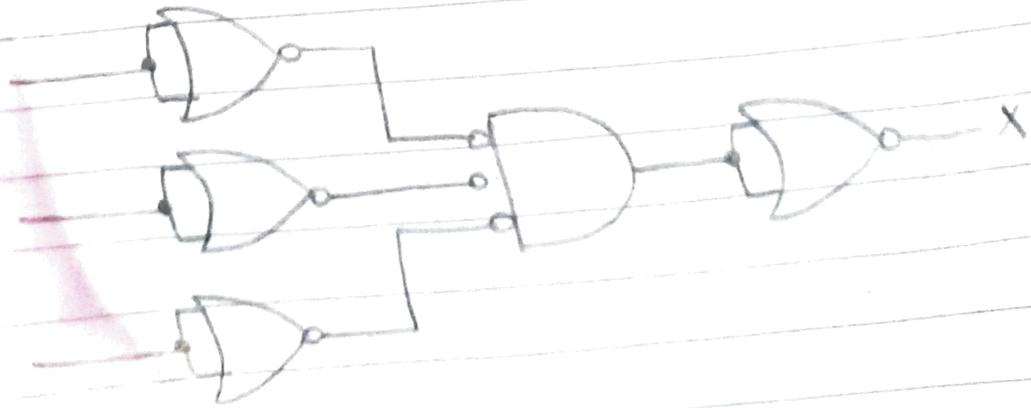


c) $X = A + B$

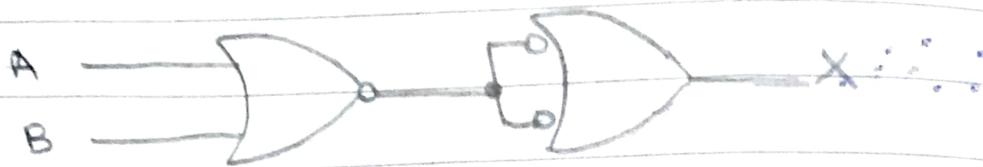


d) $X = A + B + \bar{C}$

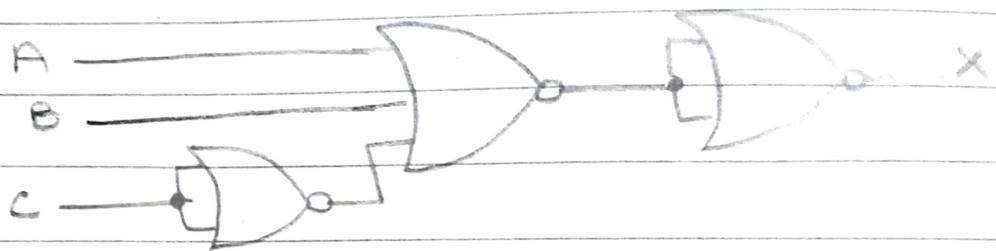

e) $X = \overline{AB} + \overline{CD}$

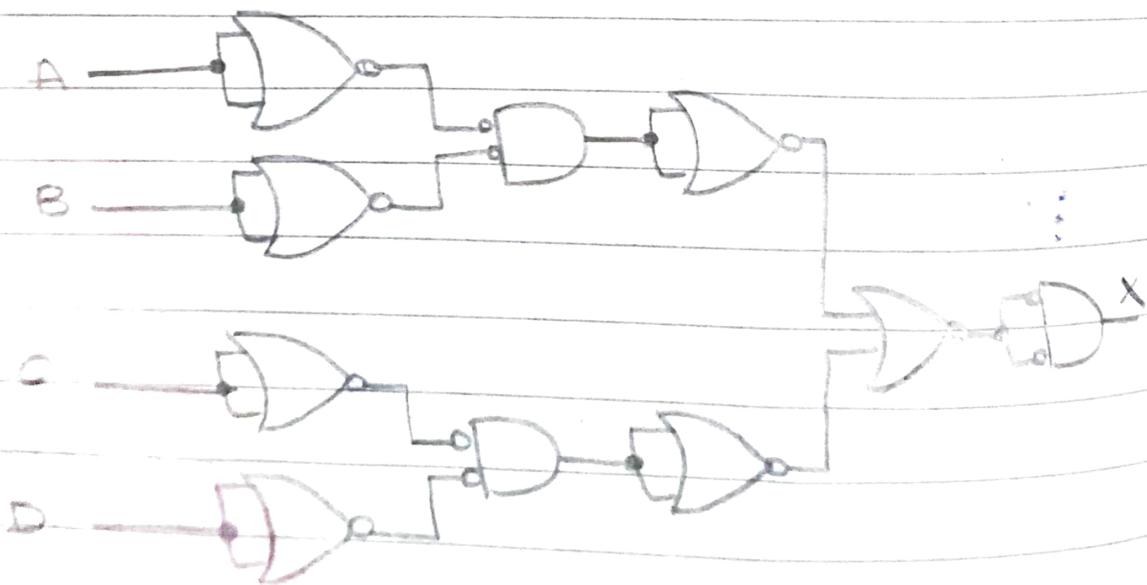


f) $X = (A+B)(C+D)$

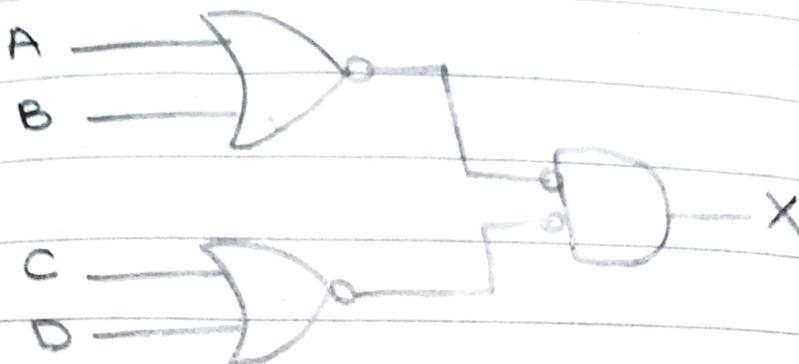

25. Repeat Problem 24 using only NAND gates.


a) $X = ABC$

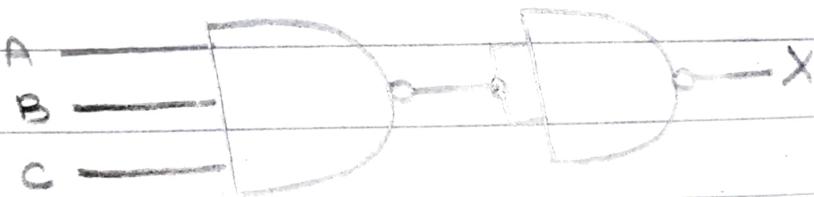


b) $X = \overline{ABC}$




c) $X = A + B$

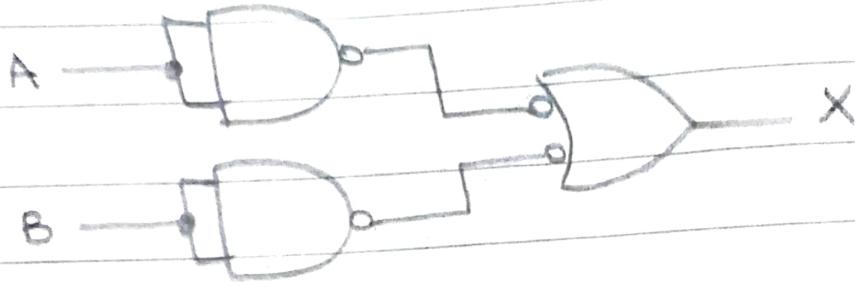


d) $X = A + B + \overline{C}$

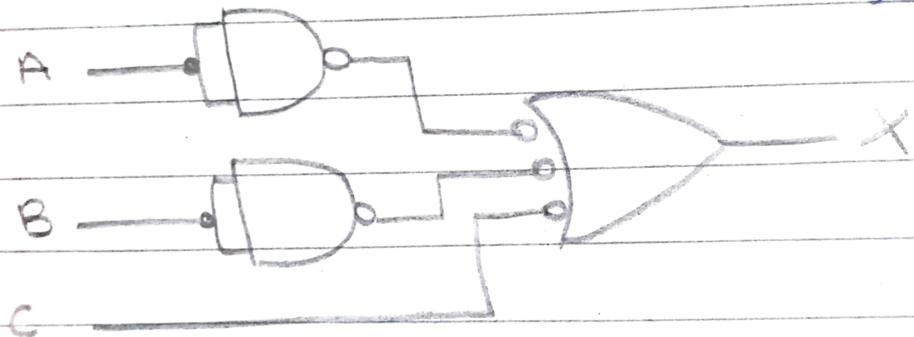

e) $X = \overline{AB} + \overline{CD}$

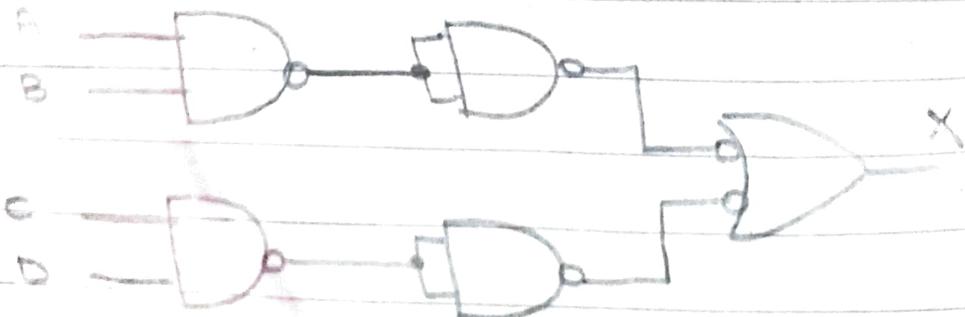


f) $X = (A+B)(C+D)$

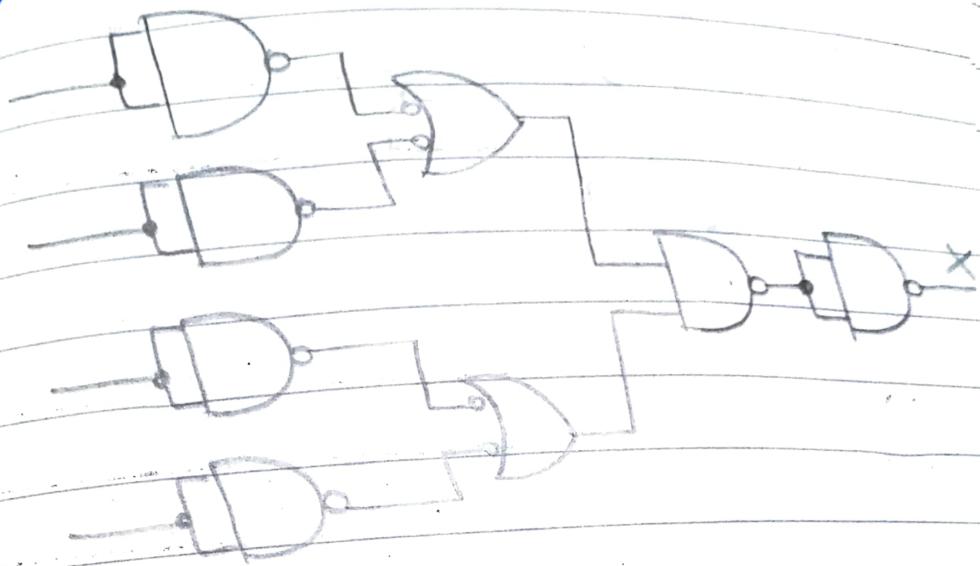


26. Implement each function
in Problem 10 by using only
NAND gates.


a) $X = AB$

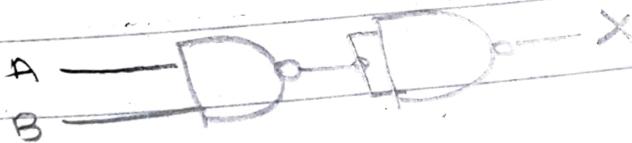


b) $X = A + B$

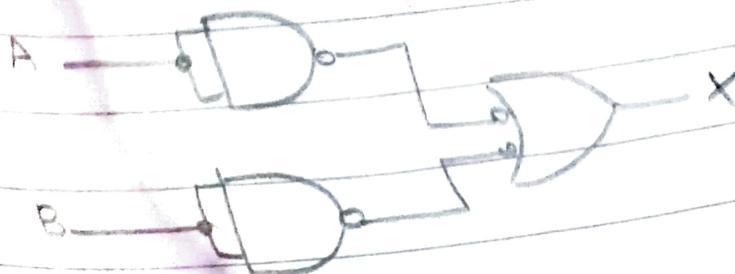


c) $X = AB + C$

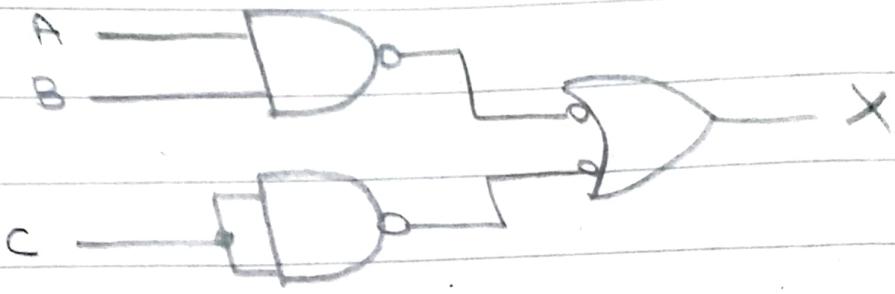


d) $X = ABC + D$

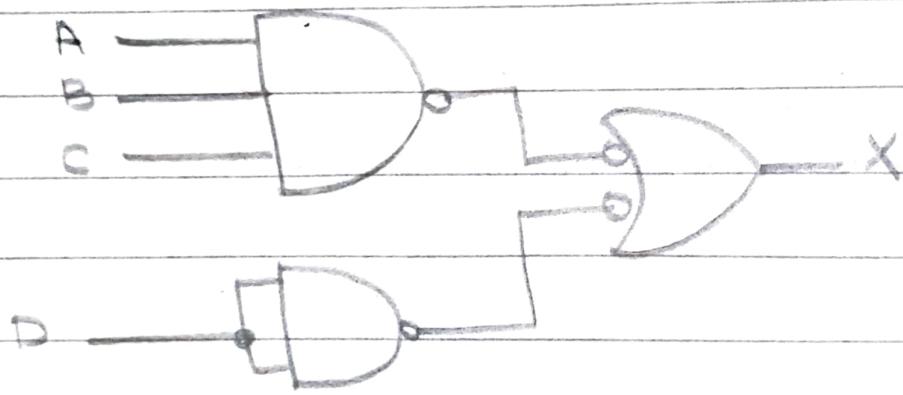

e) $X = A + B + C$

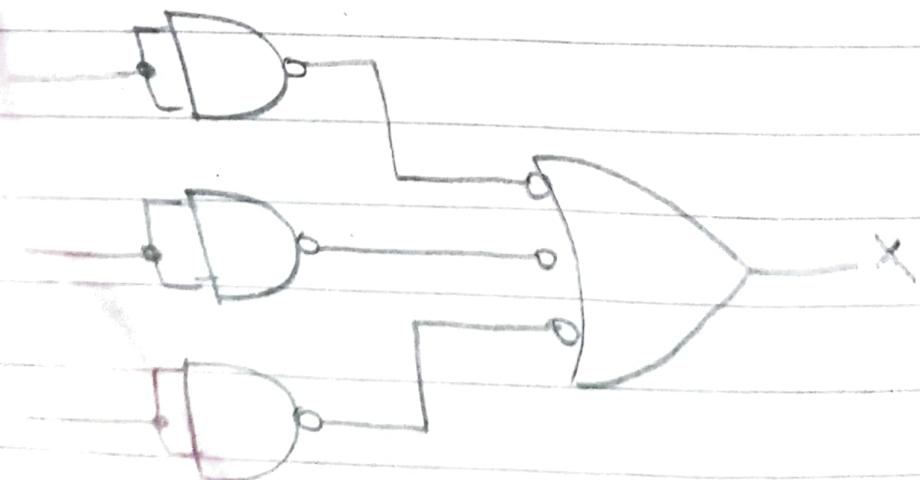


f) $X = ABCD$

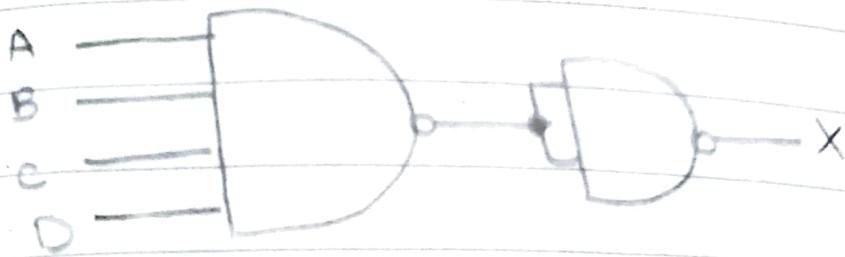


g) $X = A(CD + B)$

$$\Rightarrow X = ACD + AB$$

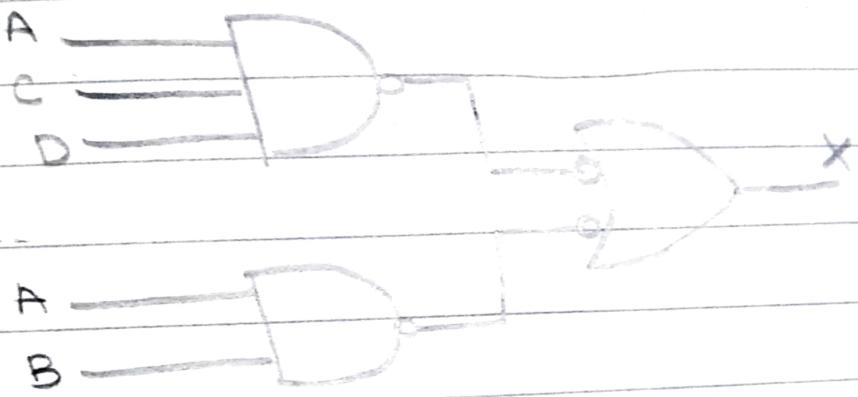


27. Implement each function
in Problem 11 by using
only NAND gates.

a) $X = AB + \bar{B}C$

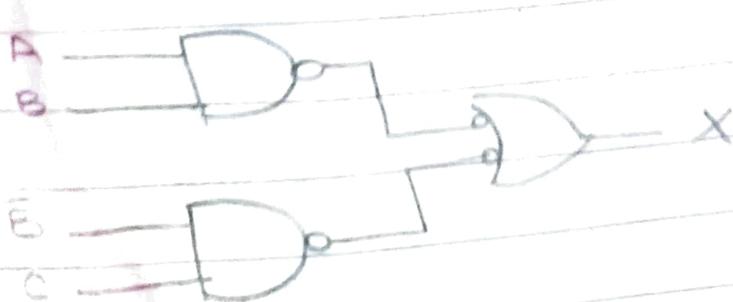


b) $X = A(B + \overline{C})$

$$X = AB + A\overline{C}$$

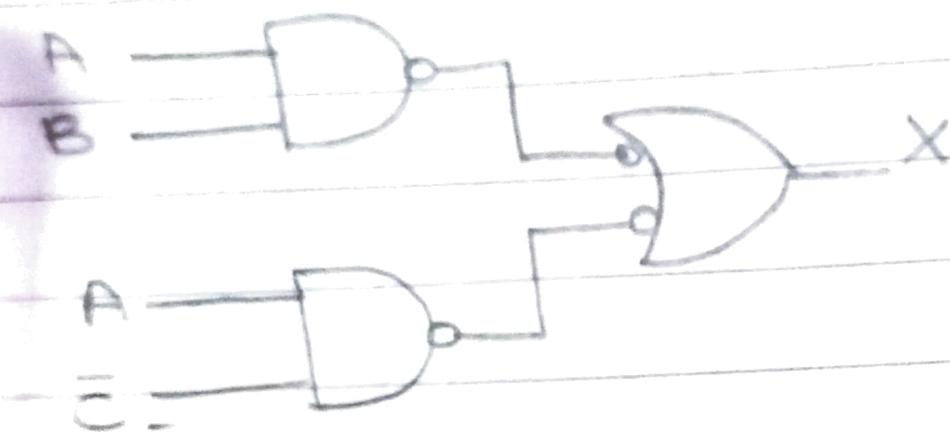


c) $X = A\overline{B} + AB$

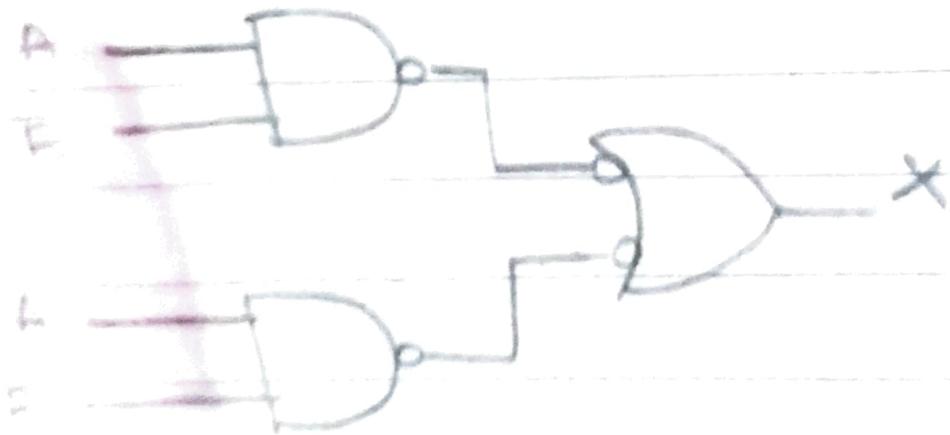

PULSE WAVEFORM OPERATION:

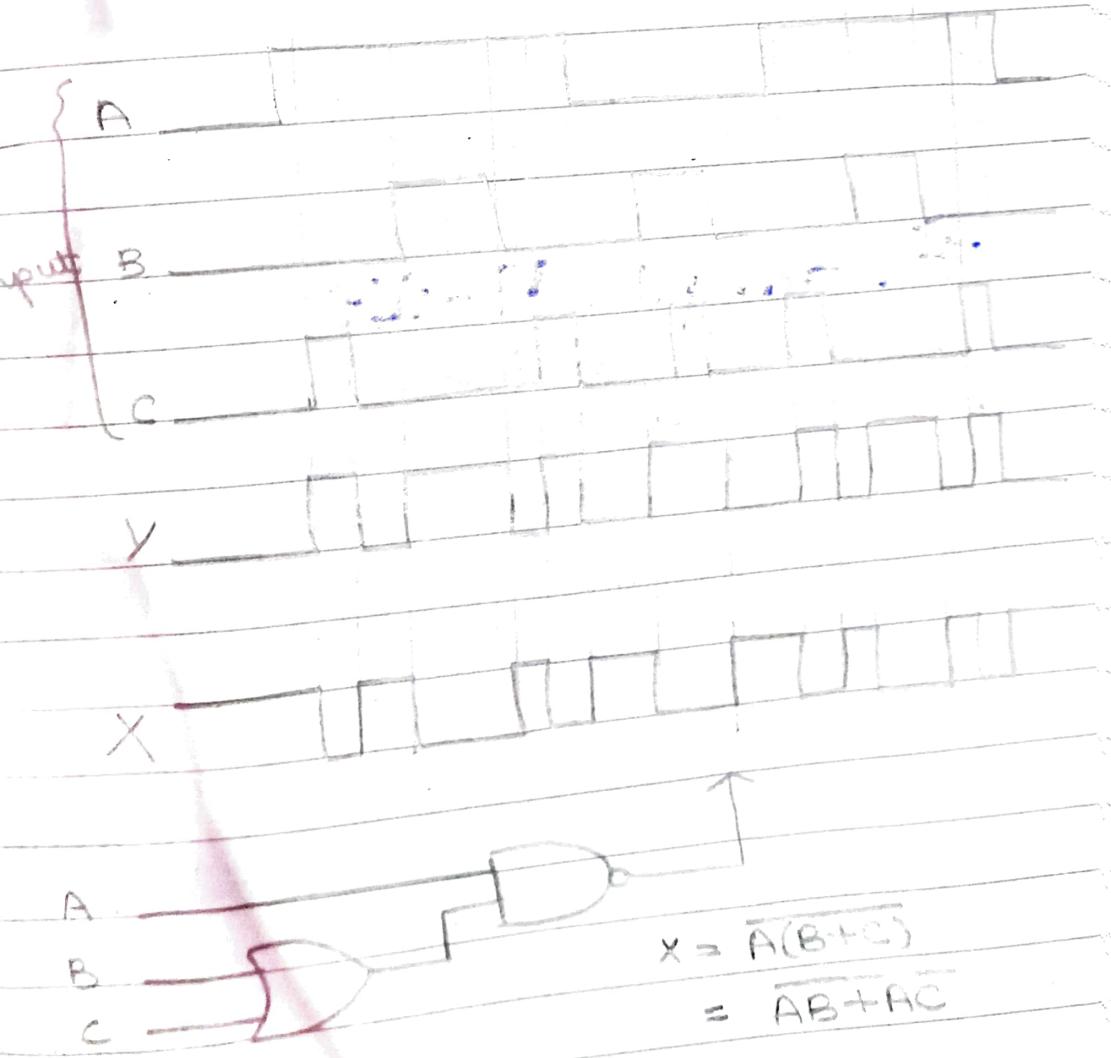Example 5-12

Determine the final output waveform X for the circuit with input waveforms A, B, C.



Solution:


The output expression $AB + AC$ indicates the output X is LOW when both A and B are HIGH or when both A and C are HIGH or when all inputs are HIGH.


The output waveform X is shown in the timing diagram.

The intermediate waveform y at the output of the OR gate is also shown.

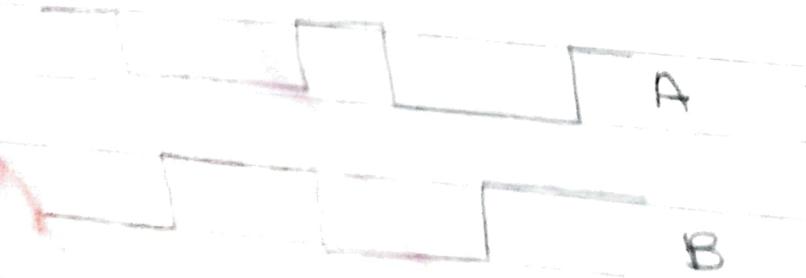Example 5-13


Draw the timing diagram for the circuit showing the outputs of G_1 , G_2 and G_3 with the input waveform A and B as indicated.



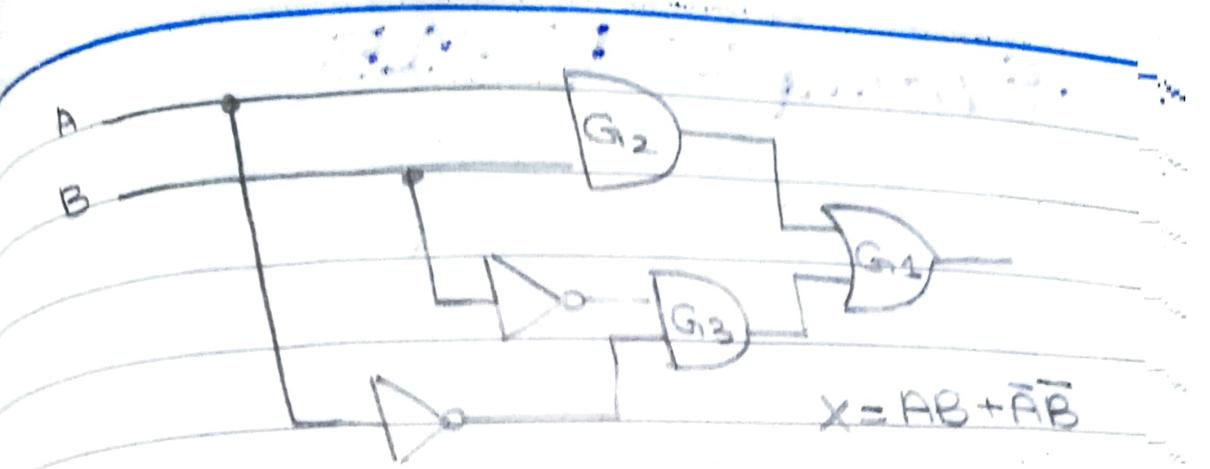

Solution:

When both inputs are HIGH or when both inputs are LOW, the output X is HIGH. Notice that this is an exclusive-NOR circuit. The intermediate outputs of gates G_{12} and G_{13} are shown in figure.

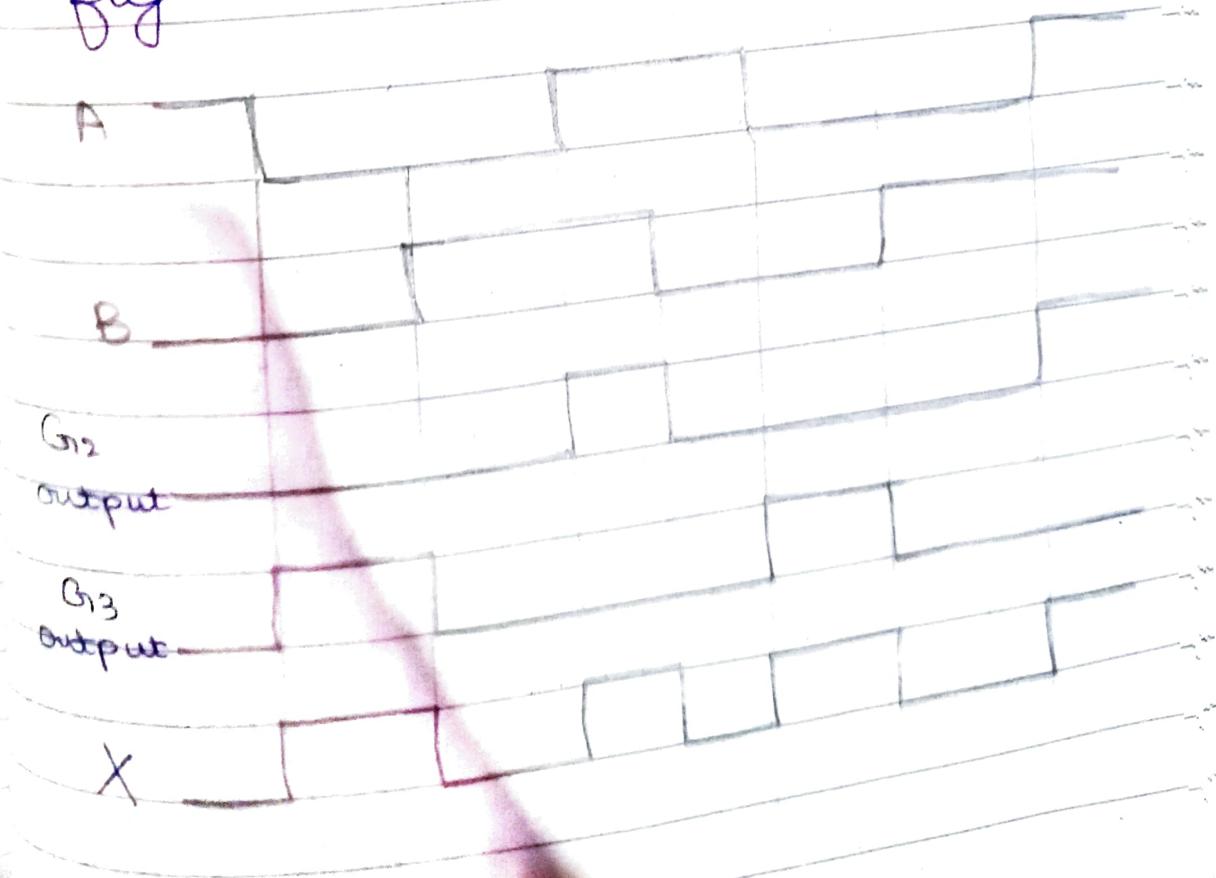


Example 5-15

Determine the output waveform X for the circuit, directly from the output expression.

Solution:

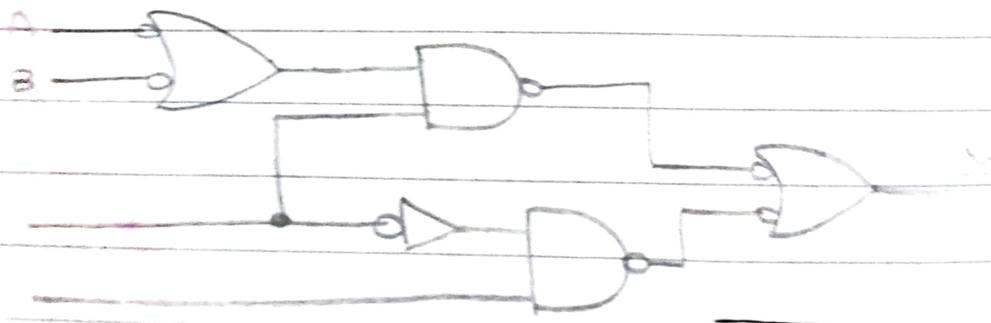
The output expression for the circuit is developed. The SOP form indicates that the output is HIGH when A is LOW and C is HIGH or when B is LOW and C is HIGH or when C is LOW and D is HIGH.



$$\begin{aligned}X &= (\overline{A} + \overline{B})C + \overline{C}\overline{D} \\&= (\overline{A} + \overline{B})C + \overline{CD} \\&= \overline{A}C + \overline{B}C + \overline{CD}\end{aligned}$$

The result is shown in figure and is the same as the one obtained by the intermediate


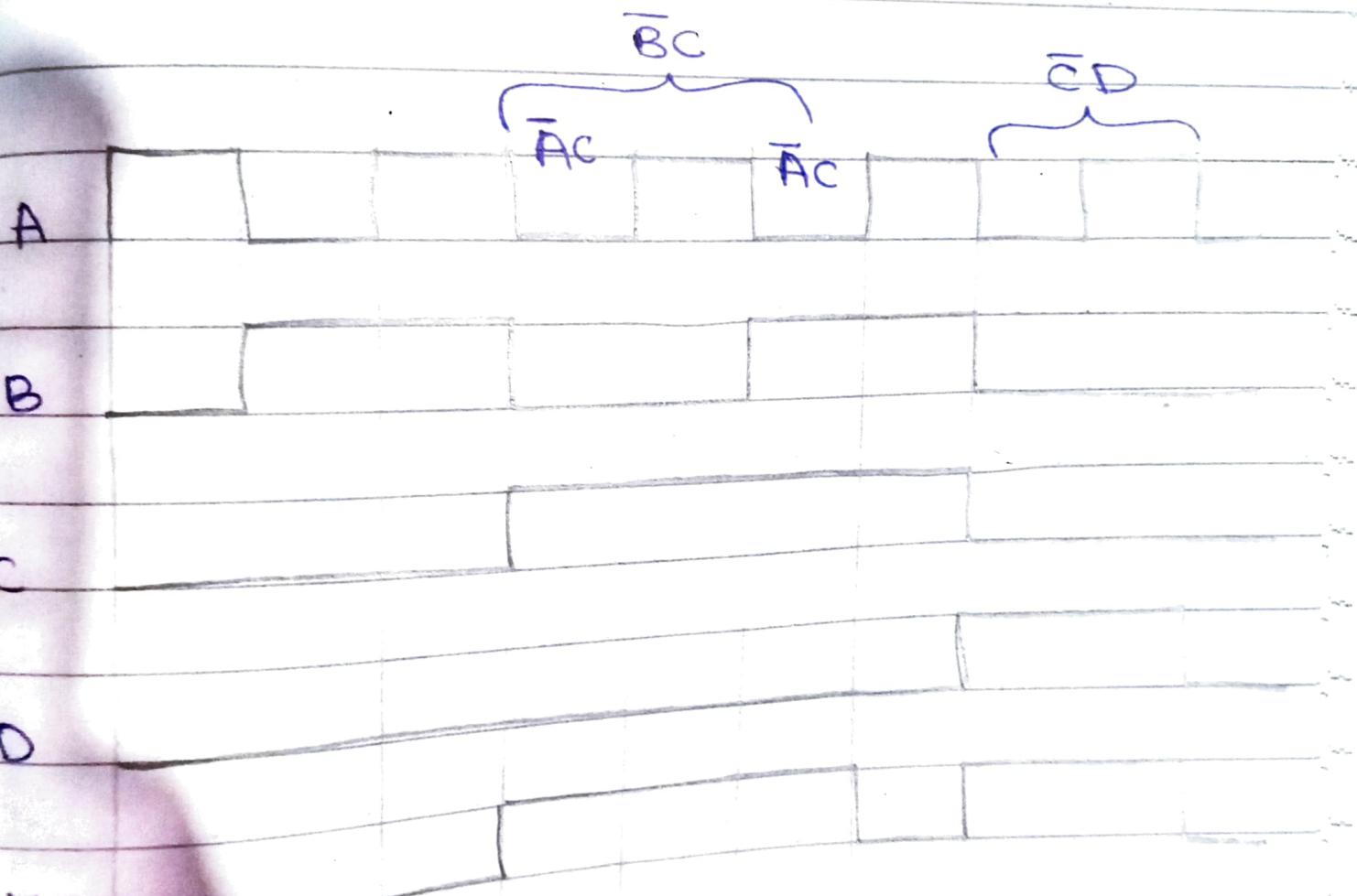
waveform method. The corresponding product terms for each waveform condition that results in a HIGH output are indicated



$$X = \bar{A}C + \bar{B}C + \bar{C}D$$

Section 5-5

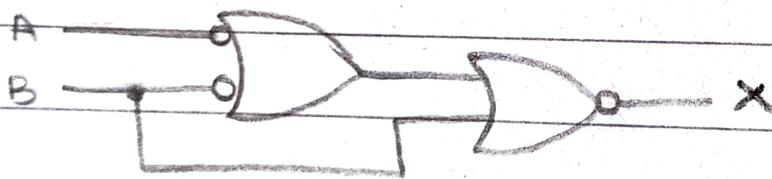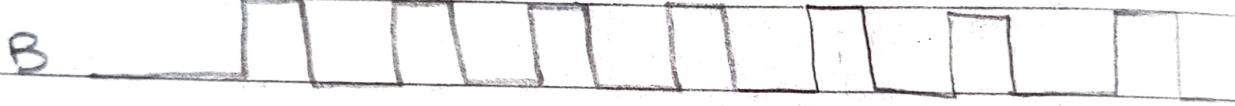
28. The output of the logic circuit and input waveforms is passed through an inverter. Draw the output waveforms.



$$\begin{aligned}\Rightarrow X &= \overline{\overline{A} + \overline{B} + B} \\ &= \overline{AB\overline{B}} \\ \Rightarrow X &= 0\end{aligned}$$

The output X is LOW.

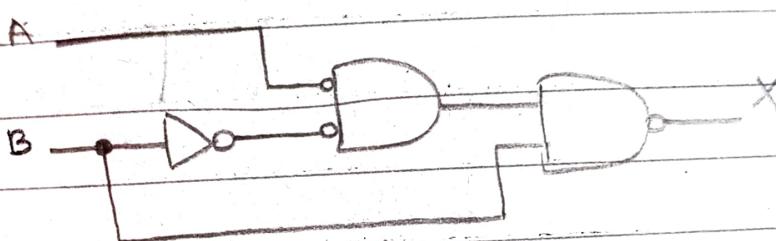
29. For the logic circuit, draw the output waveform in proper relationship to the inputs.




$$\Rightarrow X = (A\bar{B})B$$

$$= A + \bar{B} + B$$

$$= A + \bar{B}$$

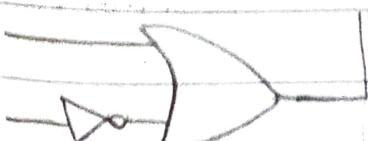

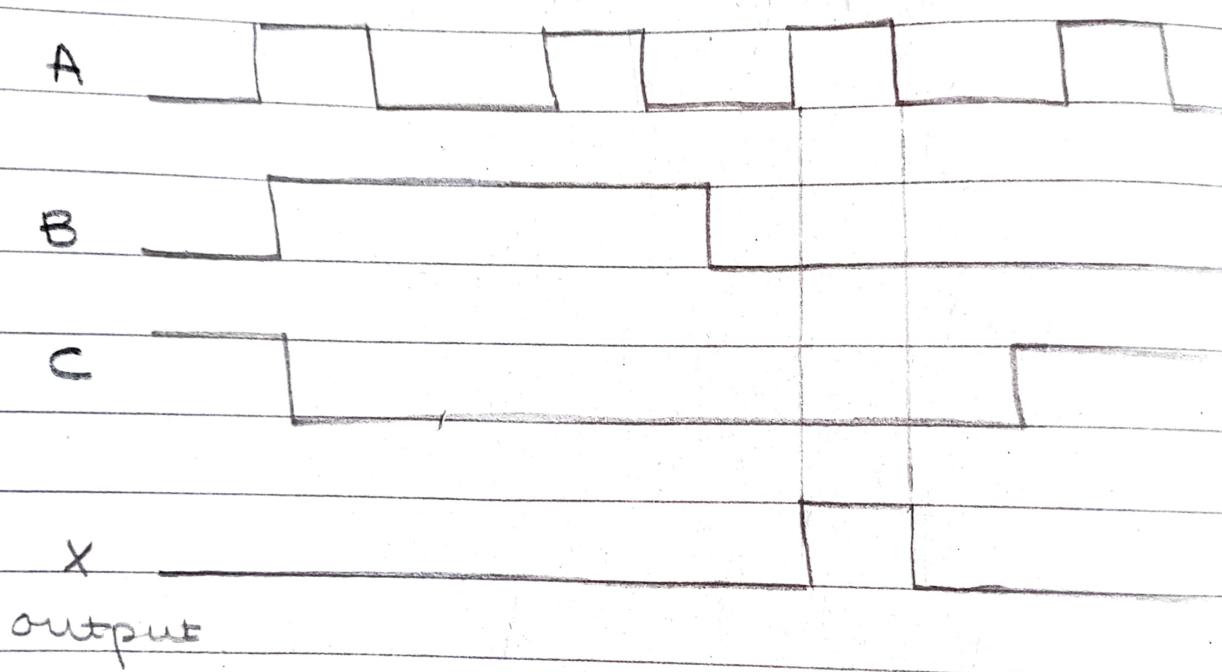31. Repeat Problem 30 for the waveforms in figure.



X is HIGH when $\star A$ is HIGH,
B is LOW and C is LOW

$$\Rightarrow X = \overline{ABC}$$

